
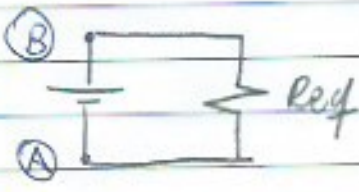
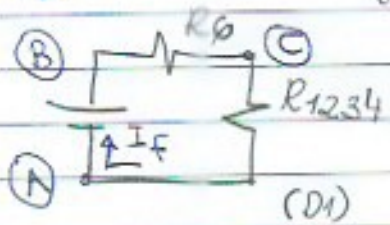
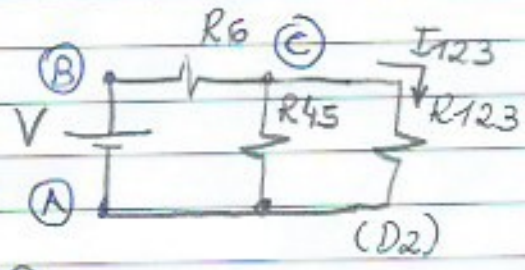
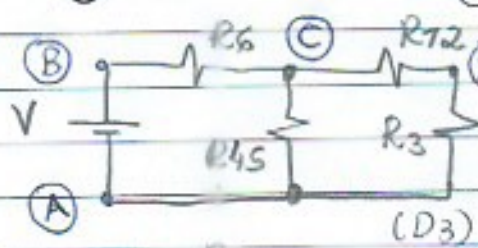


① Cálculo de potência na fonte de 32V:

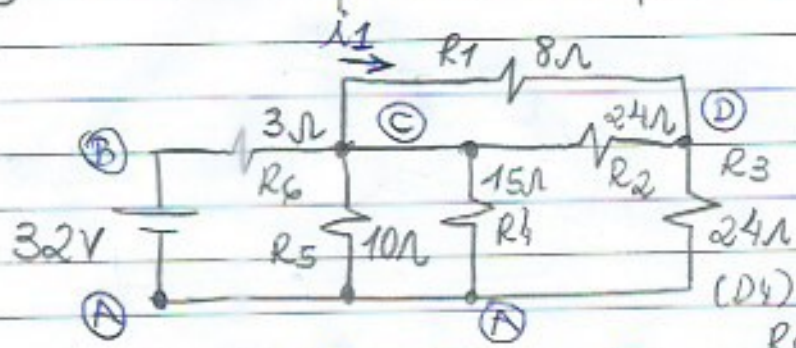

$$R_{12} = R_1 // R_2 = 6 \Omega \quad R_{45} = R_4 // R_5 = 5 \Omega$$

$$R_{123} = R_{12} + R_3 = 30 \Omega \quad R_{12345} = R_{123} // R_{45} = 5 \Omega$$

$$R_{eq} = R_6 + R_{1234} = 8 \Omega$$

$$P_f = \frac{V_f^2}{R_{eq}} = \frac{32^2}{8} = 128 \text{ W} //$$

② Cálculo de i_1 :

corrente na fonte: $I_f = \frac{V_f}{R_{eq}} = \frac{32}{8} = 4 \text{ A}$

Do desenho D1: $V_{AC} = R_{1234} \cdot I_f = 5 \cdot 4 = 20 \text{ V}$


Do desenho D2: $V_{123} = V_{AC} = 20 \text{ V}$

$$I_{123} = \frac{V_{123}}{R_{123}} = \frac{20}{30} = 0,667 \text{ A}$$

Do desenho D3: $V_{12} = V_{CD} = R_{12} \cdot I_{12} = 6 \cdot 0,667 = 4 \text{ V}$

$$I_{123} = I_{12}$$

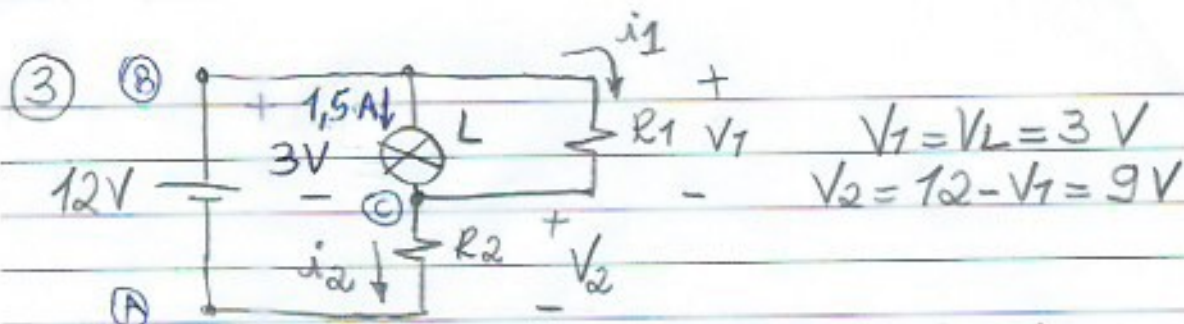
$$V_{12} = V_1 = V_2 \Rightarrow I_1 = \frac{V_1}{R_1} = \frac{4}{8} = 0,5 \text{ A} = 500 \text{ mA} //$$



Do nó ©: $1,5 + i_1 = i_2 \Rightarrow 1,5 = i_2 - i_1$
 $1,5 = \frac{V_2}{R_2} - \frac{V_1}{R_1}$ mas $R_1 = R_2 = R$, então:

$$1,5 = \frac{V_2 - V_1}{R} \Rightarrow R \cdot 1,5 = V_2 - V_1 \Rightarrow R = \frac{9 - 3}{1,5}$$

$$R = 4 \Omega //$$

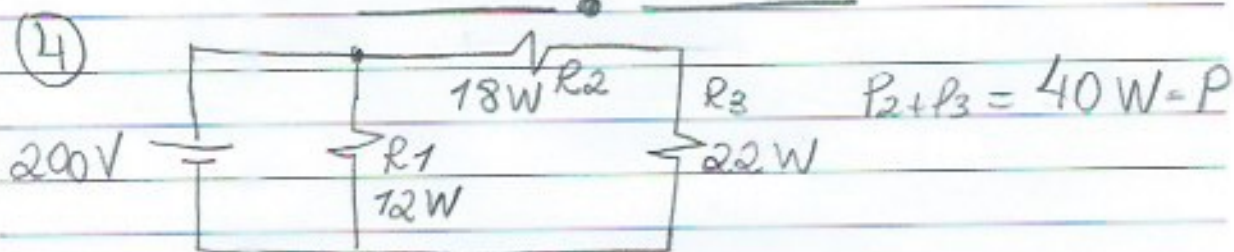

$$I_2 = I_3 = I = \frac{P}{V} = \frac{40}{200} = 0,2 \text{ A}$$

$$R_2 = \frac{P_2}{I_2^2} = \frac{18}{0,2^2} = 450 \Omega //$$

$$R_3 = \frac{P_3}{I_3^2} = \frac{22}{0,2^2} = 550 \Omega //$$

⑤ $P_t = V_{rede} \cdot I_{fusível} = 220 \cdot 16 = 3.520 \text{ W}$
 $P_{cond} = 800 \text{ W}$
 $Q_T = \frac{P_t}{P_{cond}} = \frac{3.520}{800} = 4,4 \text{ unidades}$

\Rightarrow Para não queimar o fusível = 4 und //