

Chapter 7, Solution 1.

Applying KVL to Fig. 7.1.

$$\frac{1}{C} \int_{-\infty}^t i \, dt + Ri = 0$$

Taking the derivative of each term,

$$\frac{i}{C} + R \frac{di}{dt} = 0$$

or
$$\frac{di}{i} = -\frac{dt}{RC}$$

Integrating,

$$\ln\left(\frac{i(t)}{I_0}\right) = \frac{-t}{RC}$$

$$i(t) = I_0 e^{-t/RC}$$

$$v(t) = Ri(t) = RI_0 e^{-t/RC}$$

or
$$\underline{v(t) = V_0 e^{-t/RC}}$$

Chapter 7, Solution 2.

$$\tau = R_{th} C$$

where R_{th} is the Thevenin equivalent at the capacitor terminals.

$$R_{th} = 120 \parallel 80 + 12 = 60 \, \Omega$$

$$\tau = 60 \times 0.5 \times 10^{-3} = \underline{\underline{30 \, \text{ms}}}$$

Chapter 7, Solution 3.

$$(a) \quad R_{Th} = 10 \parallel 10 = 5k\Omega, \quad \tau = R_{Th} C = 5 \times 10^3 \times 2 \times 10^{-6} = \underline{10 \, \text{ms}}$$

$$(b) \quad R_{Th} = 20 \parallel (5 + 25) + 8 = 20\Omega, \quad \tau = R_{Th} C = 20 \times 0.3 = \underline{6s}$$

Chapter 7, Solution 4.

$$\tau = R_{eq} C_{eq}$$

$$\text{where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}, \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\tau = \frac{R_1 R_2 C_1 C_2}{(R_1 + R_2)(C_1 + C_2)}$$

Chapter 7, Solution 5.

$$v(t) = v(4)e^{-(t-4)/\tau}$$

where $v(4) = 24$, $\tau = RC = (20)(0.1) = 2$


$$v(t) = 24e^{-(t-4)/2}$$
$$v(10) = 24e^{-6/2} = \underline{\underline{1.195 \text{ V}}}$$

Chapter 7, Solution 6.

$$v_o = v(0) = \frac{2}{10+2}(24) = 4 \text{ V}$$
$$v(t) = v_o e^{-t/\tau}, \quad \tau = RC = 40 \times 10^{-6} \times 2 \times 10^3 = \frac{2}{25}$$
$$v(t) = \underline{\underline{4e^{-12.5t} \text{ V}}}$$

Chapter 7, Solution 7.

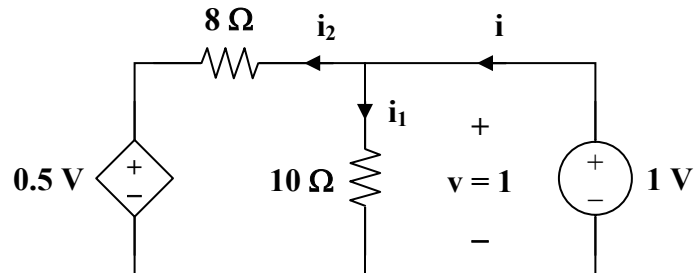$v(t) = v(0)e^{-t/\tau}$, $\tau = R_{th}C$
where R_{th} is the Thevenin resistance across the capacitor. To determine R_{th} , we insert a 1-V voltage source in place of the capacitor as shown below.



$$i_1 = \frac{1}{10} = 0.1, \quad i_2 = \frac{1-0.5}{8} = \frac{1}{16}$$
$$i = i_1 + i_2 = 0.1 + \frac{1}{16} = \frac{13}{80}$$
$$R_{th} = \frac{1}{i} = \frac{80}{13}$$
$$\tau = R_{th}C = \frac{80}{13} \times 0.1 = \frac{8}{13}$$
$$v(t) = \underline{\underline{20e^{-13t/8} \text{ V}}}$$

Chapter 7, Solution 8.

$$(a) \quad \tau = RC = \frac{1}{4}$$

$$-i = C \frac{dv}{dt}$$

$$-0.2e^{-4t} = C(10)(-4)e^{-4t} \longrightarrow C = \underline{\underline{5 \text{ mF}}}$$

$$R = \frac{1}{4C} = \underline{\underline{50 \Omega}}$$

$$(b) \quad \tau = RC = \frac{1}{4} = \underline{\underline{0.25 \text{ s}}}$$

$$(c) \quad w_C(0) = \frac{1}{2} CV_0^2 = \frac{1}{2} (5 \times 10^{-3})(100) = \underline{\underline{250 \text{ mJ}}}$$

$$(d) \quad w_R = \frac{1}{2} \times \frac{1}{2} CV_0^2 = \frac{1}{2} CV_0^2 (1 - e^{-2t_0/\tau})$$

$$0.5 = 1 - e^{-8t_0} \longrightarrow e^{-8t_0} = \frac{1}{2}$$

$$\text{or} \quad e^{8t_0} = 2$$

$$t_0 = \frac{1}{8} \ln(2) = \underline{\underline{86.6 \text{ ms}}}$$

Chapter 7, Solution 9.


$$v(t) = v(0)e^{-t/\tau}, \quad \tau = R_{\text{eq}}C$$

$$R_{\text{eq}} = 2 + 8 \parallel 8 + 6 \parallel 3 = 2 + 4 + 2 = 8 \Omega$$

$$\tau = R_{\text{eq}}C = (0.25)(8) = 2$$

$$v(t) = \underline{\underline{20e^{-t/2} \text{ V}}}$$

Chapter 7, Solution 10.

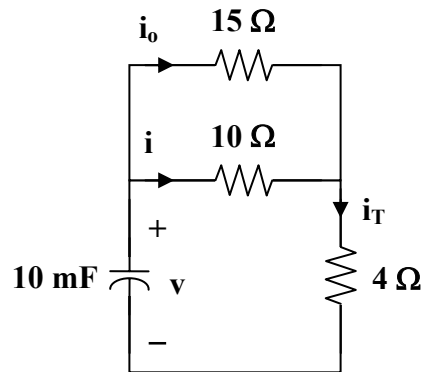

$$15i_o = 10i \longrightarrow i_o = \frac{(10)(3)}{15} = 2 \text{ A}$$

i.e. if $i(0) = 3 \text{ A}$, then $i_o(0) = 2 \text{ A}$

$$i_T(0) = i(0) + i_o(0) = 5 \text{ A}$$

$$v(0) = 10i(0) + 4i_T(0) = 30 + 20 = 50 \text{ V}$$

across the capacitor terminals.

$$R_{th} = 4 + 10 \parallel 15 = 4 + 6 = 10 \Omega$$

$$\tau = R_{th}C = (10)(10 \times 10^{-3}) = 0.1$$

$$v(t) = v(0)e^{-t/\tau} = 50e^{-10t}$$

$$i_C = C \frac{dv}{dt} = (10 \times 10^{-3})(-500e^{-10t})$$

$$i_C = -5e^{-10t} \text{ A}$$

By applying the current division principle,

$$i(t) = \frac{15}{10+15}(-i_C) = -0.6i_C = \underline{\underline{3e^{-10t} \text{ A}}}$$

Chapter 7, Solution 11.

Applying KCL to the RL circuit,

$$\frac{1}{L} \int v dt + \frac{v}{R} = 0$$

Differentiating both sides,

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} = 0 \longrightarrow \frac{dv}{dt} + \frac{R}{L}v = 0$$

$$v = Ae^{-Rt/L}$$

If the initial current is I_0 , then

$$v(0) = I_0 R = A$$

$$v = I_0 R e^{-t/\tau}, \quad \tau = \frac{L}{R}$$

$$i = \frac{1}{L} \int_{-\infty}^t v(t) dt$$



$$i = \frac{-\tau I_0 R}{L} e^{-t/\tau} \Big|_{-\infty}^t$$

$$i = -I_0 R e^{-t/\tau}$$

$$\underline{i(t) = I_0 e^{-t/\tau}}$$

Chapter 7, Solution 12.

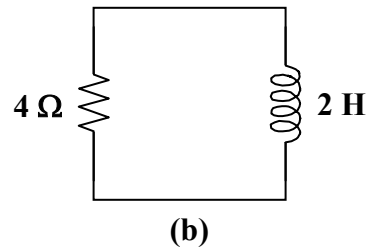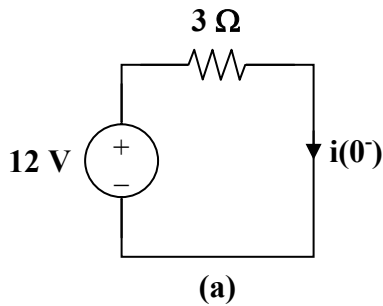When $t < 0$, the switch is closed and the inductor acts like a short circuit to dc. The 4Ω resistor is short-circuited so that the resulting circuit is as shown in Fig. (a).



$$i(0^-) = \frac{12}{3} = 4 \text{ A}$$

Since the current through an inductor cannot change abruptly,

$$i(0) = i(0^-) = i(0^+) = 4 \text{ A}$$

When $t > 0$, the voltage source is cut off and we have the RL circuit in Fig. (b).

$$\tau = \frac{L}{R} = \frac{2}{4} = 0.5$$

Hence,

$$i(t) = i(0) e^{-t/\tau} = \underline{4 e^{-2t} \text{ A}}$$

Chapter 7, Solution 13.

$$\tau = \frac{L}{R_{th}}$$


where R_{th} is the Thevenin resistance at the terminals of the inductor.

$$R_{th} = 70 \parallel 30 + 80 \parallel 20 = 21 + 16 = 37 \Omega$$

$$\tau = \frac{2 \times 10^{-3}}{37} = \underline{\underline{81.08 \mu s}}$$

Chapter 7, Solution 14

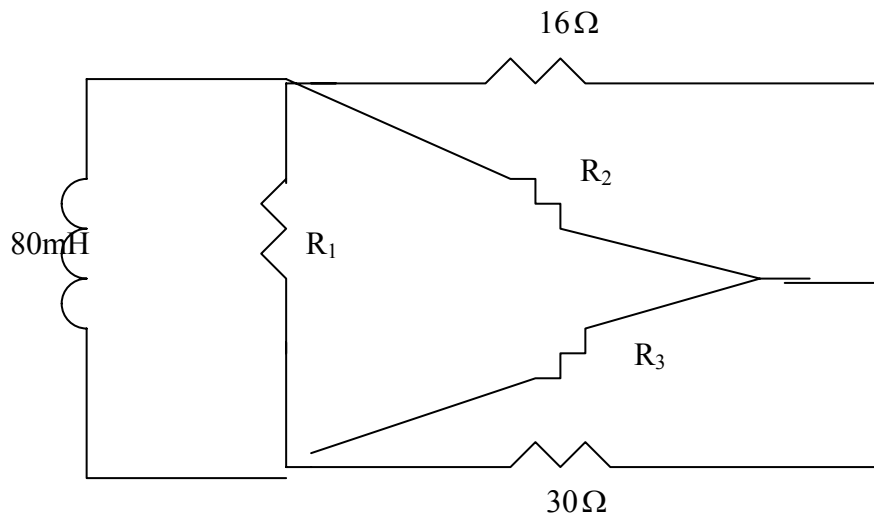Converting the wye-subnetwork to delta gives



$$R_1 = \frac{10 \times 20 + 20 \times 50 + 50 \times 10}{20} = 1700 / 20 = 85 \Omega, \quad R_2 = \frac{1700}{50} = 34 \Omega, \quad R_3 = \frac{1700}{10} = 170 \Omega$$

$$30 \parallel 170 = (30 \times 170) / 200 = 25.5 \Omega, \quad 34 \parallel 16 = (34 \times 16) / 50 = 10.88 \Omega$$

$$R_{th} = 85 \parallel (25.5 + 10.88) = \frac{85 \times 36.38}{121.38} = 25.476 \Omega, \quad \tau = \frac{L}{R_{th}} = \frac{80 \times 10^{-3}}{25.476} = \underline{\underline{3.14 ms}}$$

Chapter 7, Solution 15

$$(a) R_{Th} = 12 + 10 // 40 = 20\Omega, \quad \tau = \frac{L}{R_{Th}} = 5 / 20 = \underline{0.25s}$$

$$(b) R_{Th} = 40 // 160 + 8 = 40\Omega, \quad \tau = \frac{L}{R_{Th}} = (20 \times 10^{-3}) / 40 = \underline{0.5 \text{ ms}}$$

Chapter 7, Solution 16.

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$(a) \quad L_{eq} = L \text{ and } R_{eq} = R_2 + \frac{R_1 R_3}{R_1 + R_3} = \frac{R_2(R_1 + R_3) + R_1 R_3}{R_1 + R_3}$$

$$\tau = \frac{L(R_1 + R_3)}{R_2(R_1 + R_3) + R_1 R_3}$$

$$(b) \quad \text{where } L_{eq} = \frac{L_1 L_2}{L_1 + L_2} \text{ and } R_{eq} = R_3 + \frac{R_1 R_2}{R_1 + R_2} = \frac{R_3(R_1 + R_2) + R_1 R_2}{R_1 + R_2}$$

$$\tau = \frac{L_1 L_2 (R_1 + R_2)}{(L_1 + L_2)(R_3(R_1 + R_2) + R_1 R_2)}$$

Chapter 7, Solution 17.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R_{eq}} = \frac{1/4}{4} = \frac{1}{16}$$


$$i(t) = 2e^{-16t}$$

$$v_o(t) = 3i + L \frac{di}{dt} = 6e^{-16t} + (1/4)(-16)2e^{-16t}$$

$$v_o(t) = \underline{-2e^{-16t} \text{ V}}$$

Chapter 7, Solution 18.

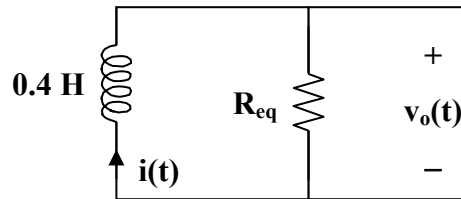If $v(t) = 0$, the circuit can be redrawn as shown below.




$$R_{eq} = 2 \parallel 3 = \frac{6}{5}, \quad \tau = \frac{L}{R} = \frac{2}{5} \times \frac{5}{6} = \frac{1}{3}$$

$$i(t) = i(0)e^{-t/\tau} = e^{-3t}$$

$$v_o(t) = -L \frac{di}{dt} = \frac{-2}{5} (-3)e^{-3t} = \underline{\underline{1.2e^{-3t} \text{ V}}}$$

Chapter 7, Solution 19.

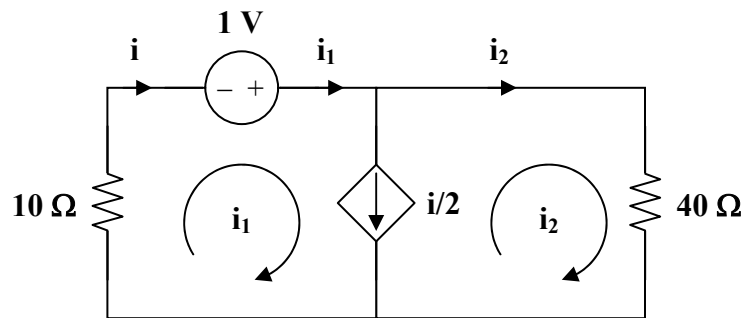

To find R_{th} we replace the inductor by a 1-V voltage source as shown above.

$$10i_1 - 1 + 40i_2 = 0$$

But $i = i_2 + i/2$ and $i = i_1$

i.e. $i_1 = 2i_2 = 2i$

$$10i - 1 + 20i = 0 \longrightarrow i = \frac{1}{30}$$

$$R_{th} = \frac{1}{i} = 30 \Omega$$

$$\tau = \frac{L}{R_{th}} = \frac{6}{30} = 0.2 \text{ s}$$


$$i(t) = \underline{\underline{2e^{-5t} \text{ A}}}$$

Chapter 7, Solution 20.

- (a). $\tau = \frac{L}{R} = \frac{1}{50} \longrightarrow R = 50L$
 $-v = L \frac{di}{dt}$
 $-150e^{-50t} = L(30)(-50)e^{-50t} \longrightarrow L = \underline{\underline{0.1 \text{ H}}}$
 $R = 50L = \underline{\underline{5 \Omega}}$
- (b). $\tau = \frac{L}{R} = \frac{1}{50} = \underline{\underline{20 \text{ ms}}}$
- (c). $w = \frac{1}{2}Li^2(0) = \frac{1}{2}(0.1)(30)^2 = \underline{\underline{45 \text{ J}}}$
- (d). Let p be the fraction
 $\frac{1}{2}LI_0 \cdot p = \frac{1}{2}LI_0(1 - e^{-2t_0/\tau})$
 $p = 1 - e^{-(2)(10)/50} = 1 - e^{-0.4} = 0.3296$
 i.e. $p = \underline{\underline{33\%}}$

Chapter 7, Solution 21.

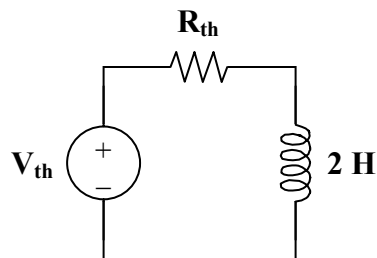The circuit can be replaced by its Thevenin equivalent shown below.



$$V_{th} = \frac{80}{80 + 40}(60) = 40 \text{ V}$$

$$R_{th} = 40 \parallel 80 + R = \frac{80}{3} + R$$

$$I = i(0) = i(\infty) = \frac{V_{th}}{R_{th}} = \frac{40}{80/3 + R}$$

$$w = \frac{1}{2}LI^2 = \frac{1}{2}(2)\left(\frac{40}{R + 80/3}\right)^2 = 1$$

$$\frac{40}{R + 80/3} = 1 \longrightarrow R = \frac{40}{3}$$

$$R = \underline{\underline{13.33 \Omega}}$$

Chapter 7, Solution 22.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R_{\text{eq}}}$$

$$R_{\text{eq}} = 5 \parallel 20 + 1 = 5 \Omega, \quad \tau = \frac{2}{5}$$

$$i(t) = \underline{\mathbf{10e^{-2.5t} \text{ A}}}$$

Using current division, the current through the 20 ohm resistor is

$$i_o = \frac{5}{5+20}(-i) = \frac{-i}{5} = -2e^{-2.5t}$$

$$v(t) = 20i_o = \underline{\mathbf{-40e^{-2.5t} \text{ V}}}$$

Chapter 7, Solution 23.

Since the 2 Ω resistor, 1/3 H inductor, and the (3+1) Ω resistor are in parallel, they always have the same voltage.

$$-i = \frac{2}{2} + \frac{2}{3+1} = 1.5 \longrightarrow i(0) = -1.5$$

The Thevenin resistance R_{th} at the inductor's terminals is

$$R_{\text{th}} = 2 \parallel (3+1) = \frac{4}{3}, \quad \tau = \frac{L}{R_{\text{th}}} = \frac{1/3}{4/3} = \frac{1}{4}$$

$$i(t) = i(0)e^{-t/\tau} = -1.5e^{-4t}, \quad t > 0$$

$$v_L = v_o = L \frac{di}{dt} = -1.5(-4)(1/3)e^{-4t}$$

$$v_o = \underline{\mathbf{2e^{-4t} \text{ V}, \quad t > 0}}$$

$$v_x = \frac{1}{3+1}v_L = \underline{\mathbf{0.5e^{-4t} \text{ V}, \quad t > 0}}$$

Chapter 7, Solution 24.

$$(a) \quad v(t) = \underline{\mathbf{-5u(t)}}$$

$$(b) \quad i(t) = -10[u(t) - u(t-3)] + 10[u(t-3) - u(t-5)]$$

$$= \underline{\mathbf{-10u(t) + 20u(t-3) - 10u(t-5)}}$$

$$\begin{aligned}
 \text{(c) } x(t) &= (t-1)[u(t-1) - u(t-2)] + [u(t-2) - u(t-3)] \\
 &\quad + (4-t)[u(t-3) - u(t-4)] \\
 &= (t-1)u(t-1) - (t-2)u(t-2) - (t-3)u(t-3) + (t-4)u(t-4) \\
 &= \underline{\underline{\mathbf{r(t-1) - r(t-2) - r(t-3) + r(t-4)}}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(d) } y(t) &= 2u(-t) - 5[u(t) - u(t-1)] \\
 &= \underline{\underline{\mathbf{2u(-t) - 5u(t) + 5u(t-1)}}}
 \end{aligned}$$

Chapter 7, Solution 25.

$$\underline{\underline{\mathbf{v(t) = [u(t) + r(t-1) - r(t-2) - 2u(t-2)] V}}}$$

Chapter 7, Solution 26.

$$\begin{aligned}
 \text{(a) } v_1(t) &= u(t+1) - u(t) + [u(t-1) - u(t)] \\
 v_1(t) &= \underline{\underline{\mathbf{u(t+1) - 2u(t) + u(t-1)}}}
 \end{aligned}$$


$$\begin{aligned}
 \text{(b) } v_2(t) &= (4-t)[u(t-2) - u(t-4)] \\
 v_2(t) &= -(t-4)u(t-2) + (t-4)u(t-4) \\
 v_2(t) &= \underline{\underline{\mathbf{2u(t-2) - r(t-2) + r(t-4)}}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(c) } v_3(t) &= 2[u(t-2) - u(t-4)] + 4[u(t-4) - u(t-6)] \\
 v_3(t) &= \underline{\underline{\mathbf{2u(t-2) + 2u(t-4) - 4u(t-6)}}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(d) } v_4(t) &= -t[u(t-1) - u(t-2)] = -tu(t-1) + tu(t-2) \\
 v_4(t) &= (-t+1-1)u(t-1) + (t-2+2)u(t-2) \\
 v_4(t) &= \underline{\underline{\mathbf{-r(t-1) - u(t-1) + r(t-2) + 2u(t-2)}}}
 \end{aligned}$$


Chapter 7, Solution 27.

$v(t)$ is sketched below.

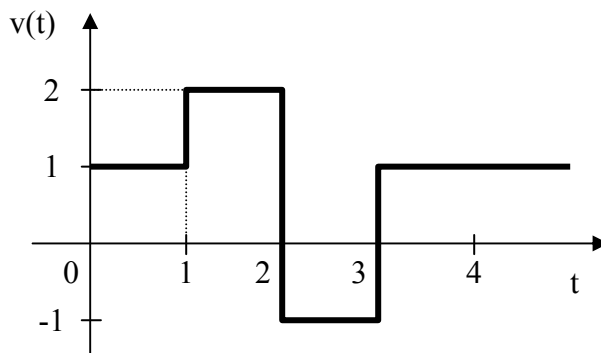


Chapter 7, Solution 28.

$i(t)$ is sketched below.

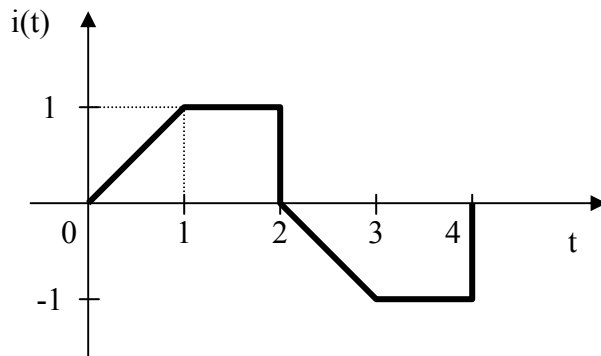


Chapter 7, Solution 29


(a)

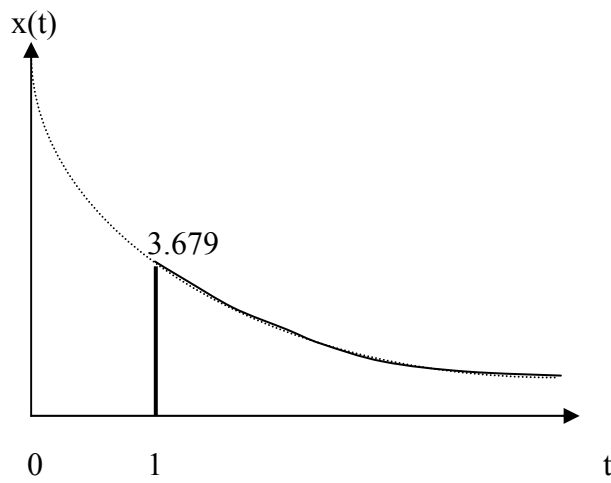

(b)

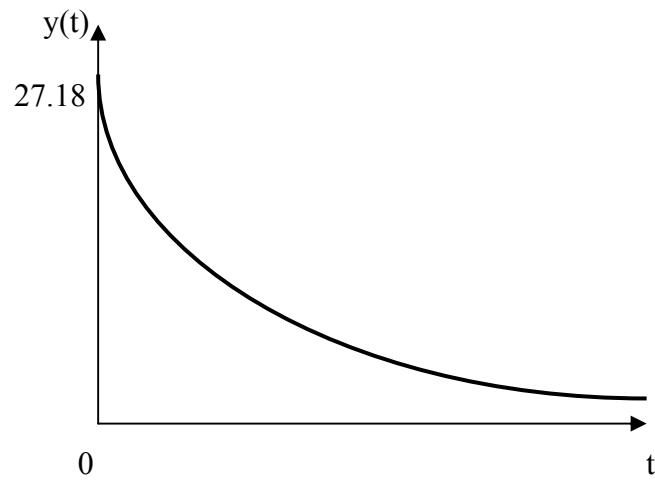

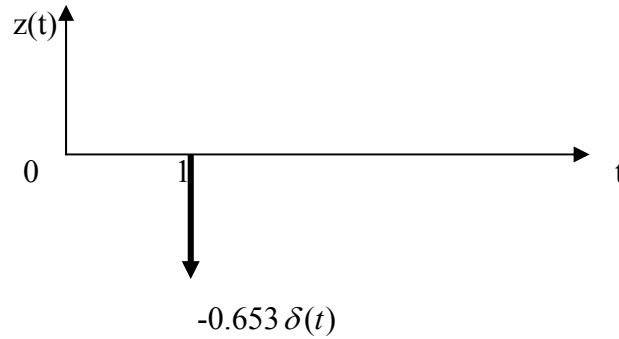(c) $z(t) = \cos 4t \delta(t-1) = \cos 4\delta(t-1) = -0.6536\delta(t-1)$, which is sketched below.



Chapter 7, Solution 30.

$$(a) \int_0^{10} 4t^2 \delta(t-1) dt = 4t^2 \Big|_{t=1} = \underline{4}$$

$$(b) \int_{-\infty}^{\infty} \cos(2\pi t) \delta(t-0.5) dt = \cos(2\pi t) \Big|_{t=0.5} = \cos \pi = \underline{-1}$$

Chapter 7, Solution 31.

$$(a) \int_{-\infty}^{\infty} [e^{-4t^2} \delta(t-2)] dt = e^{-4t^2} \Big|_{t=2} = e^{-16} = \underline{112 \times 10^{-9}}$$

$$(b) \int_{-\infty}^{\infty} [5\delta(t) + e^{-t} \delta(t) + \cos 2\pi t \delta(t)] dt = (5 + e^{-t} + \cos(2\pi t)) \Big|_{t=0} = 5 + 1 + 1 = \underline{7}$$

Chapter 7, Solution 32.

$$(a) \int_1^t u(\lambda) d\lambda = \int_1^t 1 d\lambda = \lambda \Big|_1^t = \underline{t-1}$$

$$(b) \int_0^4 r(t-1) dt = \int_0^1 0 dt + \int_1^4 (t-1) dt = \frac{t^2}{2} - t \Big|_1^4 = \underline{4.5}$$

$$(c) \int_1^5 (t-6)^2 \delta(t-2) dt = (t-6)^2 \Big|_{t=2} = \underline{16}$$

Chapter 7, Solution 33.

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0)$$

$$i(t) = \frac{10^{-3}}{10 \times 10^{-3}} \int_0^t 20\delta(t-2) dt + 0$$

$$i(t) = \underline{\mathbf{2u(t-2) A}}$$

Chapter 7, Solution 34.

$$(a) \quad \frac{d}{dt} [u(t-1)u(t+1)] = \delta(t-1)u(t+1) + u(t-1)\delta(t+1) = \delta(t-1) \bullet 1 + 0 \bullet \delta(t+1) = \underline{\delta(t-1)}$$

$$(b) \quad \frac{d}{dt} [r(t-6)u(t-2)] = u(t-6)u(t-2) + r(t-6)\delta(t-2) = u(t-6) \bullet 1 + 0 \bullet \delta(t-2) = \underline{u(t-6)}$$

$$(c) \quad \frac{d}{dt} [\sin 4t u(t-3)] = 4 \cos 4t u(t-3) + \sin 4t \delta(t-3) \\ = 4 \cos 4t u(t-3) + \sin 4 \times 3 \delta(t-3) \\ = \underline{4 \cos 4t u(t-3) - 0.5366 \delta(t-3)}$$

Chapter 7, Solution 35.

$$(a) \quad v(t) = A e^{-5t/3}, \quad v(0) = A = -2 \\ v(t) = \underline{\mathbf{-2e^{-5t/3} V}}$$

$$(b) \quad v(t) = A e^{2t/3}, \quad v(0) = A = 5 \\ v(t) = \underline{\mathbf{5e^{2t/3} V}}$$

Chapter 7, Solution 36.

$$\begin{aligned} \text{(a)} \quad v(t) &= A + Be^{-t}, \quad t > 0 \\ A = 1, \quad v(0) = 0 = 1 + B & \quad \text{or} \quad B = -1 \\ v(t) &= \underline{1 - e^{-t} \text{ V}, \quad t > 0} \end{aligned}$$
$$\begin{aligned} \text{(b)} \quad v(t) &= A + Be^{t/2}, \quad t > 0 \\ A = -3, \quad v(0) = -6 = -3 + B & \quad \text{or} \quad B = -3 \\ v(t) &= \underline{-3(1 + e^{t/2}) \text{ V}, \quad t > 0} \end{aligned}$$

Chapter 7, Solution 37.

Let $v = v_h + v_p$, $v_p = 10$.

$$\dot{v}_h + \frac{1}{4}v_h = 0 \quad \longrightarrow \quad v_h = Ae^{-t/4}$$

$$v = 10 + Ae^{-0.25t}$$

$$v(0) = 2 = 10 + A \quad \longrightarrow \quad A = -8$$

$$v = 10 - 8e^{-0.25t}$$

$$\text{(a)} \quad \tau = \underline{4s}$$

$$\text{(b)} \quad v(\infty) = \underline{10 \text{ V}}$$

$$\text{(c)} \quad \underline{v = 10 - 8e^{-0.25t}}$$

Chapter 7, Solution 38

Let $i = i_p + i_h$

$$\dot{i}_h + 3i_h = 0 \quad \longrightarrow \quad i_h = Ae^{-3t}u(t)$$

$$\text{Let } i_p = ku(t), \quad \dot{i}_p = 0, \quad 3ku(t) = 2u(t) \quad \longrightarrow \quad k = \frac{2}{3}$$

$$i_p = \frac{2}{3}u(t)$$

$$i = (Ae^{-3t} + \frac{2}{3})u(t)$$

If $i(0) = 0$, then $A + 2/3 = 0$, i.e. $A = -2/3$. Thus

$$\underline{i = \frac{2}{3}(1 - e^{-3t})u(t)}$$

Chapter 7, Solution 39.

(a) Before $t = 0$,

$$v(t) = \frac{1}{4+1}(20) = \underline{4 \text{ V}}$$

After $t = 0$,

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$\tau = RC = (4)(2) = 8, \quad v(0) = 4, \quad v(\infty) = 20$$

$$v(t) = 20 + (8 - 20)e^{-t/8}$$

$$v(t) = \underline{20 - 12e^{-t/8} \text{ V}}$$

(b) Before $t = 0$, $v = v_1 + v_2$, where v_1 is due to the 12-V source and v_2 is due to the 2-A source.

$$v_1 = 12 \text{ V}$$


To get v_2 , transform the current source as shown in Fig. (a).

$$v_2 = -8 \text{ V}$$


Thus,

$$v = 12 - 8 = \underline{4 \text{ V}}$$

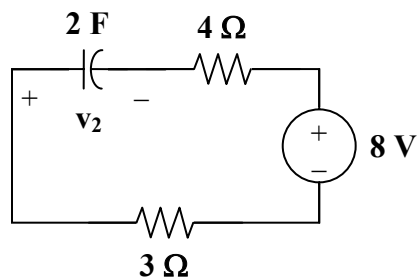After $t = 0$, the circuit becomes that shown in Fig. (b).



(a)

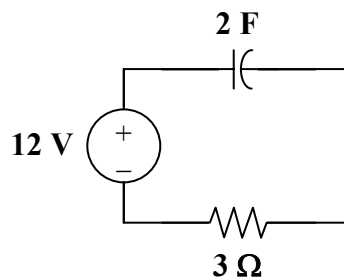

(b)

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(\infty) = 12, \quad v(0) = 4, \quad \tau = RC = (2)(3) = 6$$

$$v(t) = 12 + (4 - 12)e^{-t/6}$$

$$v(t) = \underline{12 - 8e^{-t/6} \text{ V}}$$

Chapter 7, Solution 40.

(a) Before $t = 0$, $v = \underline{12 \text{ V}}$.

After $t = 0$, $v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$


$$v(\infty) = 4, \quad v(0) = 12, \quad \tau = RC = (2)(3) = 6$$

$$v(t) = 4 + (12 - 4)e^{-t/6}$$

$$v(t) = \underline{4 + 8e^{-t/6} \text{ V}}$$

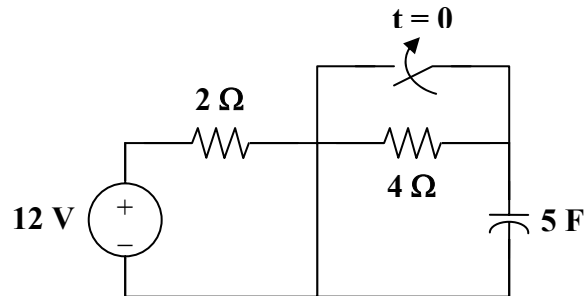(b) Before $t = 0$, $v = \underline{12 \text{ V}}$.

After $t = 0$, $v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$
 After transforming the current source, the circuit is shown below.



$$v(0) = 12, \quad v(\infty) = 12, \quad \tau = RC = (2)(5) = 10$$

$$v = \underline{12 \text{ V}}$$

Chapter 7, Solution 41.

$$v(0) = 0, \quad v(\infty) = \frac{30}{16}(12) = 10$$

$$R_{\text{eq}}C = (6 \parallel 30)(1) = \frac{(6)(30)}{36} = 5$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(t) = 10 + (0 - 10)e^{-t/5}$$

$$v(t) = \underline{10(1 - e^{-0.2t}) \text{ V}}$$

Chapter 7, Solution 42.

$$(a) \quad v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)] e^{-t/\tau}$$

$$v_o(0) = 0, \quad v_o(\infty) = \frac{4}{4+2} (12) = 8$$

$$\tau = R_{eq} C_{eq}, \quad R_{eq} = 2 \parallel 4 = \frac{4}{3}$$

$$\tau = \frac{4}{3} (3) = 4$$

$$v_o(t) = 8 - 8e^{-t/4}$$

$$v_o(t) = \underline{\underline{8(1 - e^{-0.25t}) \text{ V}}}$$

$$(b) \quad \text{For this case, } v_o(\infty) = 0 \text{ so that}$$

$$v_o(t) = v_o(0) e^{-t/\tau}$$

$$v_o(0) = \frac{4}{4+2} (12) = 8, \quad \tau = RC = (4)(3) = 12$$

$$v_o(t) = \underline{\underline{8e^{-t/12} \text{ V}}}$$

Chapter 7, Solution 43.

Before $t = 0$, the circuit has reached steady state so that the capacitor acts like an open circuit. The circuit is equivalent to that shown in Fig. (a) after transforming the voltage source.

$$0.5i = 2 - \frac{v_o}{40}, \quad i = \frac{v_o}{80}$$


$$\text{Hence, } \frac{1}{2} \frac{v_o}{80} = 2 - \frac{v_o}{40} \longrightarrow v_o = \frac{320}{5} = 64$$

$$i = \frac{v_o}{80} = \underline{\underline{0.8 \text{ A}}}$$

After $t = 0$, the circuit is as shown in Fig. (b).

$$v_C(t) = v_C(0) e^{-t/\tau}, \quad \tau = R_{th} C$$

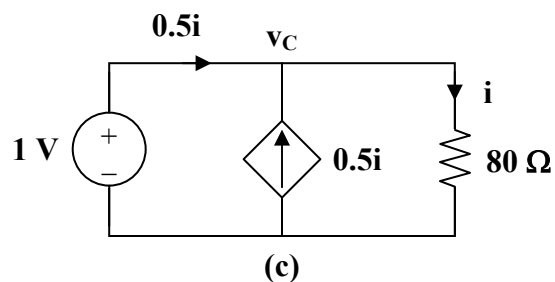To find R_{th} , we replace the capacitor with a 1-V voltage source as shown in Fig. (c).



$$i = \frac{v_C}{80} = \frac{1}{80}, \quad i_o = 0.5i = \frac{0.5}{80}$$

$$R_{th} = \frac{1}{i_o} = \frac{80}{0.5} = 160 \Omega, \quad \tau = R_{th}C = 480$$

$$v_C(0) = 64 \text{ V}$$

$$v_C(t) = 64 e^{-t/480}$$

$$0.5i = -i_C = -C \frac{dv_C}{dt} = -3 \left(\frac{1}{480} \right) 64 e^{-t/480}$$

$$i(t) = \underline{\underline{0.8 e^{-t/480} \text{ A}}}$$

Chapter 7, Solution 44.

$$R_{eq} = 6 \parallel 3 = 2 \Omega, \quad \tau = RC = 4$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

Using voltage division,

$$v(0) = \frac{3}{3+6} (30) = 10 \text{ V}, \quad v(\infty) = \frac{3}{3+6} (12) = 4 \text{ V}$$

Thus,

$$v(t) = 4 + (10 - 4) e^{-t/4} = 4 + 6 e^{-t/4}$$

$$i(t) = C \frac{dv}{dt} = (2)(6) \left(\frac{-1}{4} \right) e^{-t/4} = \underline{\underline{-3 e^{-0.25t} \text{ A}}}$$

Chapter 7, Solution 45.

$$\text{For } t < 0, v_s = 5u(t) = 0 \longrightarrow v(0) = 0$$

$$\text{For } t > 0, v_s = 5, \quad v(\infty) = \frac{4}{4+12} (5) = \frac{5}{4}$$

$$R_{eq} = 7 + 4 \parallel 12 = 10, \quad \tau = R_{eq}C = (10)(1/2) = 5$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$v(t) = \underline{\underline{1.25(1 - e^{-t/5}) \text{ V}}}$$

$$i(t) = C \frac{dv}{dt} = \left(\frac{1}{2} \right) \left(\frac{-5}{4} \right) \left(\frac{-1}{5} \right) e^{-t/5}$$

$$i(t) = \underline{\underline{0.125 e^{-t/5} \text{ A}}}$$

Chapter 7, Solution 46.

$$\tau = R_{Th}C = (2 + 6) \times 0.25 = 2s, \quad v(0) = 0, \quad v(\infty) = 6i_s = 6 \times 5 = 30$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = \underline{30(1 - e^{-t/2})} \text{ V}$$

Chapter 7, Solution 47.

$$\text{For } t < 0, \quad u(t) = 0, \quad u(t-1) = 0, \quad v(0) = 0$$

$$\text{For } 0 < t < 1, \quad \tau = RC = (2 + 8)(0.1) = 1$$

$$v(0) = 0, \quad v(\infty) = (8)(3) = 24$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$v(t) = 24(1 - e^{-t})$$

$$\text{For } t > 1, \quad v(1) = 24(1 - e^{-1}) = 15.17$$

$$-6 + v(\infty) - 24 = 0 \quad \longrightarrow \quad v(\infty) = 30$$

$$v(t) = 30 + (15.17 - 30)e^{-(t-1)}$$

$$v(t) = 30 - 14.83e^{-(t-1)}$$

Thus,

$$v(t) = \begin{cases} 24(1 - e^{-t}) \text{ V}, & 0 < t < 1 \\ \underline{30 - 14.83e^{-(t-1)} \text{ V}}, & t > 1 \end{cases}$$

Chapter 7, Solution 48.

$$\text{For } t < 0, \quad u(-t) = 1, \quad v(0) = 10 \text{ V}$$

$$\text{For } t > 0, \quad u(-t) = 0, \quad v(\infty) = 0$$

$$R_{th} = 20 + 10 = 30, \quad \tau = R_{th}C = (30)(0.1) = 3$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

$$v(t) = \underline{10e^{-t/3}} \text{ V}$$

$$i(t) = C \frac{dv}{dt} = (0.1) \left(\frac{-1}{3} \right) 10e^{-t/3}$$

$$i(t) = \underline{\frac{-1}{3}e^{-t/3}} \text{ A}$$

Chapter 7, Solution 49.

$$\begin{aligned}\text{For } 0 < t < 1, \quad v(0) &= 0, & v(\infty) &= (2)(4) = 8 \\ R_{\text{eq}} &= 4 + 6 = 10, & \tau &= R_{\text{eq}}C = (10)(0.5) = 5 \\ v(t) &= v(\infty) + [v(0) - v(\infty)] e^{-t/\tau} \\ v(t) &= 8(1 - e^{-t/5}) \text{ V}\end{aligned}$$

$$\begin{aligned}\text{For } t > 1, \quad v(1) &= 8(1 - e^{-0.2}) = 1.45, & v(\infty) &= 0 \\ v(t) &= v(\infty) + [v(1) - v(\infty)] e^{-(t-1)/\tau} \\ v(t) &= 1.45e^{-(t-1)/5} \text{ V}\end{aligned}$$

Thus,


$$v(t) = \begin{cases} 8(1 - e^{-t/5}) \text{ V}, & 0 < t < 1 \\ 1.45e^{-(t-1)/5} \text{ V}, & t > 1 \end{cases}$$

Chapter 7, Solution 50.

For the capacitor voltage,

$$\begin{aligned}v(t) &= v(\infty) + [v(0) - v(\infty)] e^{-t/\tau} \\ v(0) &= 0\end{aligned}$$

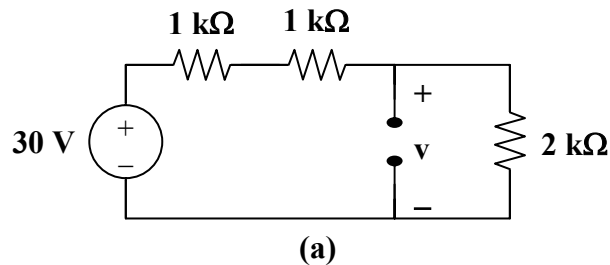For $t < 0$, we transform the current source to a voltage source as shown in Fig. (a).




$$v(\infty) = \frac{2}{2+1+1} (30) = 15 \text{ V}$$

$$R_{\text{th}} = (1+1) \parallel 2 = 1 \text{ k}\Omega$$

$$\tau = R_{\text{th}}C = 10^3 \times \frac{1}{4} \times 10^{-3} = \frac{1}{4}$$

$$v(t) = 15(1 - e^{-4t}), \quad t > 0$$

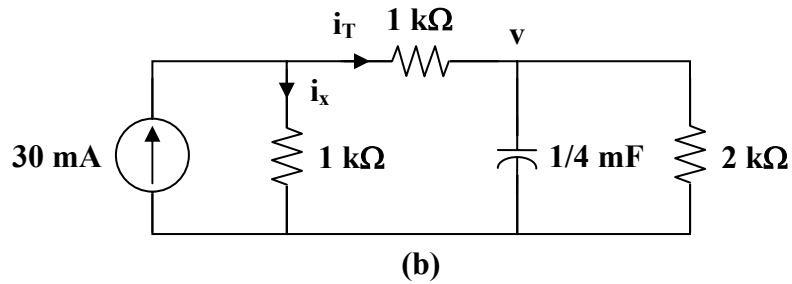We now obtain i_x from $v(t)$. Consider Fig. (b).



$$i_x = 30 \text{ mA} - i_T$$

But
$$i_T = \frac{v}{R_3} + C \frac{dv}{dt}$$

$$i_T(t) = 7.5(1 - e^{-4t}) \text{ mA} + \frac{1}{4} \times 10^{-3} (-15)(-4)e^{-4t} \text{ A}$$

$$i_T(t) = 7.5(1 + e^{-4t}) \text{ mA}$$


Thus,

$$i_x(t) = 30 - 7.5 - 7.5e^{-4t} \text{ mA}$$

$$i_x(t) = \underline{7.5(3 - e^{-4t}) \text{ mA}, \quad t > 0}$$

Chapter 7, Solution 51.

Consider the circuit below.

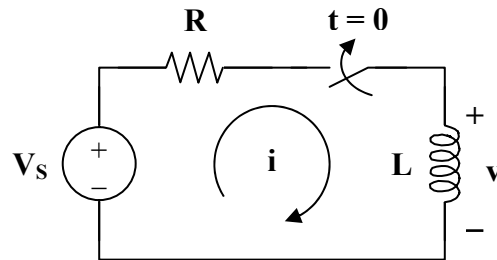

After the switch is closed, applying KVL gives

$$V_s = Ri + L \frac{di}{dt}$$

or
$$L \frac{di}{dt} = -R \left(i - \frac{V_s}{R} \right)$$

$$\frac{di}{i - V_s/R} = \frac{-R}{L} dt$$

Integrating both sides,

$$\ln\left(i - \frac{V_s}{R}\right)\Big|_{I_0}^{i(t)} = \frac{-R}{L}t$$

$$\ln\left(\frac{i - V_s/R}{I_0 - V_s/R}\right) = \frac{-t}{\tau}$$

or
$$\frac{i - V_s/R}{I_0 - V_s/R} = e^{-t/\tau}$$

$$\underline{i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-t/\tau}}$$

which is the same as Eq. (7.60).

Chapter 7, Solution 52.

$$i(0) = \frac{20}{10} = 2 \text{ A}, \quad i(\infty) = 2 \text{ A}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$\underline{i(t) = 2 \text{ A}}$$

Chapter 7, Solution 53.

(a) Before $t = 0$, $i = \frac{25}{3+2} = \underline{5 \text{ A}}$

After $t = 0$, $i(t) = i(0)e^{-t/\tau}$

$$\tau = \frac{L}{R} = \frac{4}{2} = 2, \quad i(0) = 5$$

$$\underline{i(t) = 5e^{-t/2} \text{ A}}$$

- (b) Before $t = 0$, the inductor acts as a short circuit so that the 2Ω and 4Ω resistors are short-circuited.

$$\underline{i(t) = 6 \text{ A}}$$

After $t = 0$, we have an RL circuit.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{3}{2}$$

$$\underline{i(t) = 6e^{-2t/3} \text{ A}}$$

Chapter 7, Solution 54.

- (a) Before $t = 0$, i is obtained by current division or

$$i(t) = \frac{4}{4+4} (2) = \underline{1 \text{ A}}$$

After $t = 0$,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$\tau = \frac{L}{R_{\text{eq}}}, \quad R_{\text{eq}} = 4 + 4 \parallel 12 = 7 \Omega$$

$$\tau = \frac{3.5}{7} = \frac{1}{2}$$

$$i(0) = 1, \quad i(\infty) = \frac{4 \parallel 12}{4 + 4 \parallel 12} (2) = \frac{3}{4+3} (2) = \frac{6}{7}$$

$$i(t) = \frac{6}{7} + \left(1 - \frac{6}{7}\right) e^{-2t}$$

$$i(t) = \underline{\frac{1}{7}(6 - e^{-2t}) \text{ A}}$$


- (b) Before $t = 0$, $i(t) = \frac{10}{2+3} = \underline{2 \text{ A}}$

After $t = 0$, $R_{\text{eq}} = 3 + 6 \parallel 2 = 4.5$

$$\tau = \frac{L}{R_{\text{eq}}} = \frac{2}{4.5} = \frac{4}{9}$$

$$i(0) = 2$$

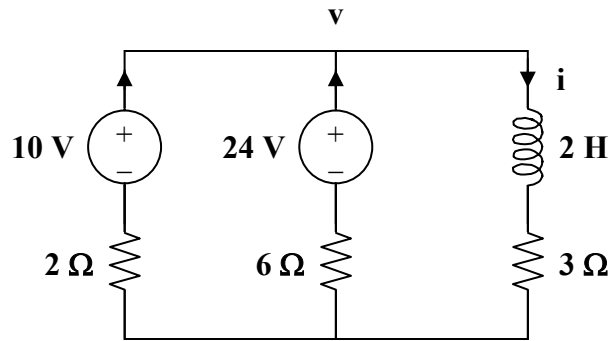To find $i(\infty)$, consider the circuit below, at $t = \infty$ when the inductor becomes a short circuit,



$$\frac{10 - v}{2} + \frac{24 - v}{6} = \frac{v}{3} \longrightarrow v = 9$$

$$i(\infty) = \frac{v}{3} = 3 \text{ A}$$

$$i(t) = 3 + (2 - 3)e^{-9t/4}$$

$$i(t) = \underline{3 - e^{-9t/4} \text{ A}}$$