



Chapter 14, Solution 1.

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\mathbf{H}(\omega) = \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}, \quad \text{where } \omega_0 = \frac{1}{RC}$$

$$H = |\mathbf{H}(\omega)| = \frac{\omega/\omega_0}{\sqrt{1 + (\omega/\omega_0)^2}} \quad \phi = \angle\mathbf{H}(\omega) = \frac{\pi}{2} - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

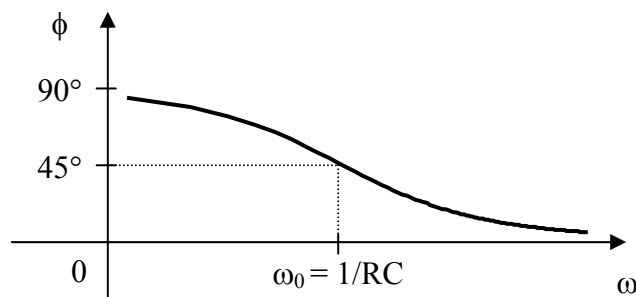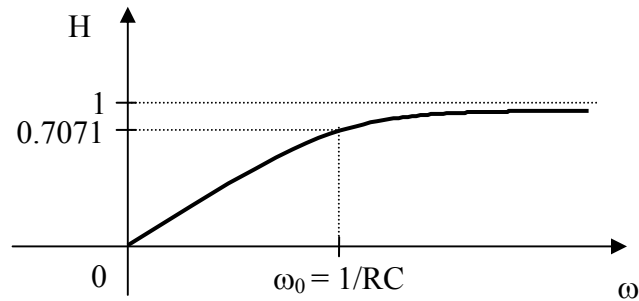This is a highpass filter. The frequency response is the same as that for P.P.14.1 except that $\omega_0 = 1/RC$. Thus, the sketches of H and ϕ are shown below.




Chapter 14, Solution 2.

$$\mathbf{H}(\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R} = \frac{1}{\underline{1 + j\omega/\omega_0}}, \quad \text{where } \underline{\omega_0 = \frac{R}{L}}$$

$$H = |\mathbf{H}(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}} \quad \phi = \angle \mathbf{H}(\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

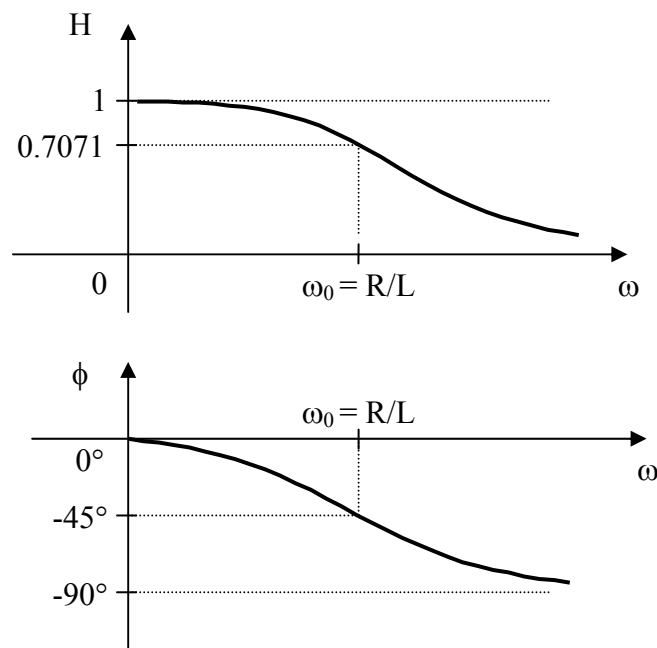The frequency response is identical to the response in Example 14.1 except that $\omega_0 = R/L$. Hence the response is shown below.




Chapter 14, Solution 3.

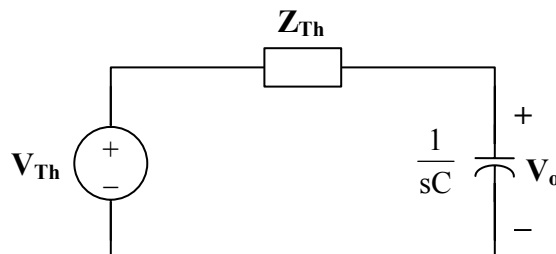- (a) The Thevenin impedance across the second capacitor where V_o is taken is

$$\mathbf{Z}_{Th} = R + R \parallel 1/sC = R + \frac{R}{1 + sRC}$$

$$\mathbf{V}_{Th} = \frac{1/sC}{R + 1/sC} \mathbf{V}_i = \frac{\mathbf{V}_i}{1 + sRC}$$



$$V_o = \frac{1/sC}{Z_{Th} + 1/sC} \cdot V_{Th} = \frac{V_i}{(1 + sRC)(1 + sCZ_{Th})}$$

$$H(s) = \frac{V_o}{V_i} = \frac{1}{(1 + sCZ_{Th})(1 + sRC)} = \frac{1}{(1 + sRC)(1 + sRC + sRC/(1 + sRC))}$$

$$H(s) = \frac{1}{\underline{s^2 R^2 C^2 + 3sRC + 1}}$$

(b) $RC = (40 \times 10^3)(2 \times 10^{-6}) = 80 \times 10^{-3} = 0.08$

There are no zeros and the poles are at

$$s_1 = \frac{-0.383}{RC} = \underline{-4.787}$$

$$s_2 = \frac{-2.617}{RC} = \underline{-32.712}$$

Chapter 14, Solution 4.

(a) $R \parallel \frac{1}{j\omega C} = \frac{R}{1 + j\omega RC}$

$$H(\omega) = \frac{V_o}{V_i} = \frac{\frac{R}{1 + j\omega RC}}{j\omega L + \frac{R}{1 + j\omega RC}} = \frac{R}{R + j\omega L(1 + j\omega RC)}$$

$$H(\omega) = \frac{R}{\underline{-\omega^2 RLC + R + j\omega L}}$$

(b) $H(\omega) = \frac{R + j\omega L}{R + j\omega L + 1/j\omega C} = \frac{j\omega C(R + j\omega L)}{1 + j\omega C(R + j\omega L)}$

$$H(\omega) = \frac{\underline{-\omega^2 LC + j\omega RC}}{\underline{1 - \omega^2 LC + j\omega RC}}$$

Chapter 14, Solution 5.

$$(a) \quad \mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{1}}{\mathbf{1 + j\omega RC - \omega^2 LC}}$$

$$(b) \quad R \parallel \frac{1}{j\omega C} = \frac{R}{1 + j\omega RC}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j\omega L}{j\omega L + R/(1 + j\omega RC)} = \frac{j\omega L(1 + j\omega RC)}{R + j\omega L(1 + j\omega RC)}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{j\omega L - \omega^2 RLC}}{\mathbf{R + j\omega L - \omega^2 RLC}}$$

Chapter 14, Solution 6.


(a) Using current division,

$$\mathbf{H}(\omega) = \frac{\mathbf{I}_o}{\mathbf{I}_i} = \frac{R}{R + j\omega L + 1/j\omega C}$$

$$\mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC - \omega^2 LC} = \frac{j\omega(20)(0.25)}{1 + j\omega(20)(0.25) - \omega^2(10)(0.25)}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{j\omega 5}}{\mathbf{1 + j\omega 5 - 2.5\omega^2}}$$

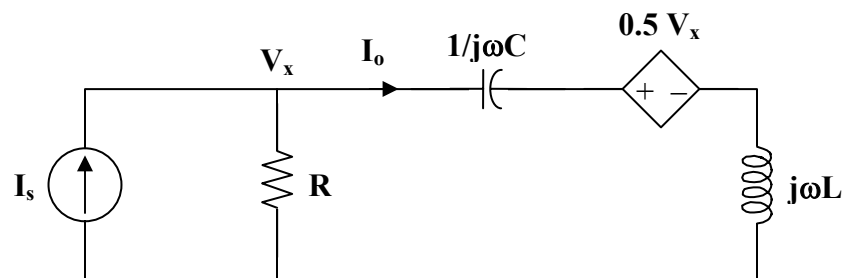(b) We apply nodal analysis to the circuit below.



$$\mathbf{I}_s = \frac{\mathbf{V}_x}{R} + \frac{\mathbf{V}_x - 0.5\mathbf{V}_x}{j\omega L + 1/j\omega C}$$

$$\text{But } \mathbf{I}_o = \frac{0.5\mathbf{V}_x}{j\omega L + 1/j\omega C} \longrightarrow \mathbf{V}_x = 2\mathbf{I}_o(j\omega L + 1/j\omega C)$$

$$\frac{\mathbf{I}_s}{\mathbf{V}_x} = \frac{1}{R} + \frac{0.5}{j\omega L + 1/j\omega C}$$

$$\frac{\mathbf{I}_s}{2\mathbf{I}_o(j\omega L + 1/j\omega C)} = \frac{1}{R} + \frac{1}{2(j\omega L + 1/j\omega C)}$$

$$\frac{\mathbf{I}_s}{\mathbf{I}_o} = \frac{2(j\omega L + 1/j\omega C)}{R} + 1$$

$$\mathbf{H}(\omega) = \frac{\mathbf{I}_o}{\mathbf{I}_s} = \frac{1}{1 + 2(j\omega L + 1/j\omega C)/R} = \frac{j\omega RC}{j\omega RC + 2(1 - \omega^2 LC)}$$

$$\mathbf{H}(\omega) = \frac{j\omega}{j\omega + 2(1 - \omega^2 \cdot 0.25)}$$

$$\mathbf{H}(\omega) = \frac{j\omega}{\underline{2 + j\omega - 0.5\omega^2}}$$

Chapter 14, Solution 7.

$$\begin{aligned} \text{(a)} \quad 0.05 &= 20 \log_{10} H \\ 2.5 \times 10^{-3} &= \log_{10} H \\ H &= 10^{2.5 \times 10^{-3}} = \underline{\underline{1.005773}} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad -6.2 &= 20 \log_{10} H \\ -0.31 &= \log_{10} H \\ H &= 10^{-0.31} = \underline{\underline{0.4898}} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad 104.7 &= 20 \log_{10} H \\ 5.235 &= \log_{10} H \\ H &= 10^{5.235} = \underline{\underline{1.718 \times 10^5}} \end{aligned}$$

Chapter 14, Solution 8.

(a) $H = 0.05$
 $H_{dB} = 20 \log_{10} 0.05 = \underline{-26.02}$, $\phi = \underline{0^\circ}$

(b) $H = 125$
 $H_{dB} = 20 \log_{10} 125 = \underline{41.94}$, $\phi = \underline{0^\circ}$

(c) $H(1) = \frac{j10}{2+j} = 4.472 \angle 63.43^\circ$
 $H_{dB} = 20 \log_{10} 4.472 = \underline{13.01}$, $\phi = \underline{63.43^\circ}$

(d) $H(1) = \frac{3}{1+j} + \frac{6}{2+j} = 3.9 - j1.7 = 4.254 \angle -23.55^\circ$
 $H_{dB} = 20 \log_{10} 4.254 = \underline{12.577}$, $\phi = \underline{-23.55^\circ}$


Chapter 14, Solution 9.

$$H(\omega) = \frac{1}{(1+j\omega)(1+j\omega/10)}$$

$$H_{dB} = -20 \log_{10} |1+j\omega| - 20 \log_{10} |1+j\omega/10|$$



$$\phi = -\tan^{-1}(\omega) - \tan^{-1}(\omega/10)$$

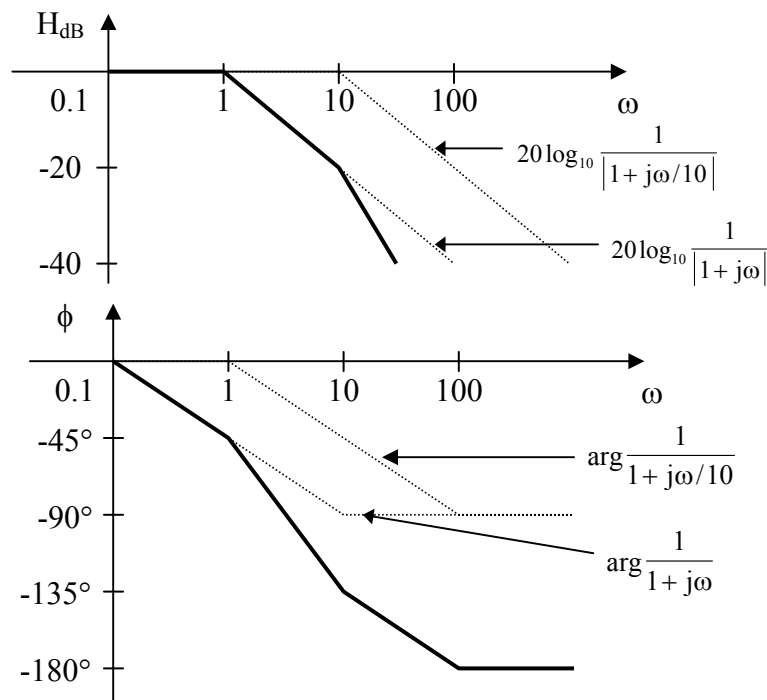The magnitude and phase plots are shown below.



Chapter 14, Solution 10.
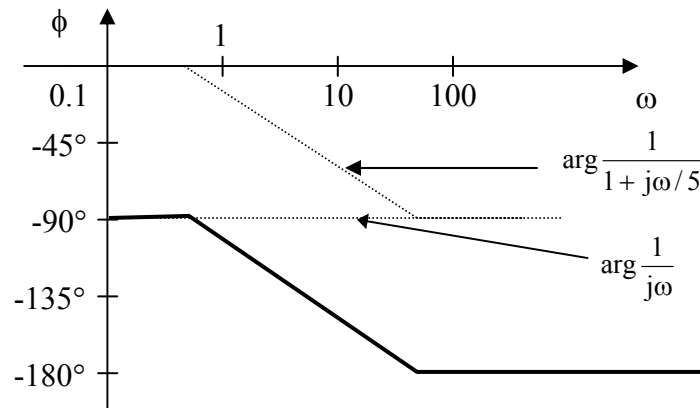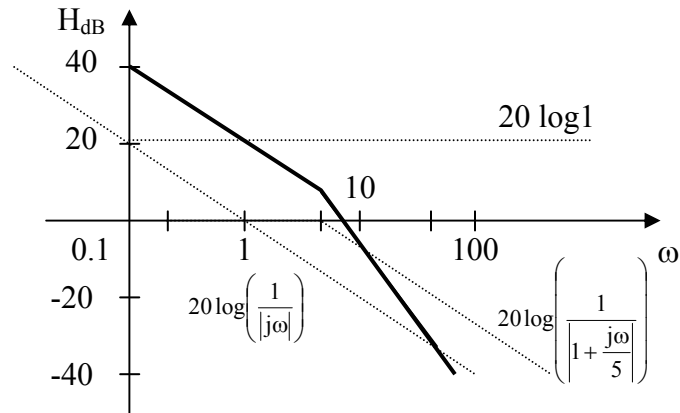
$$H(j\omega) = \frac{50}{j\omega(5 + j\omega)} = \frac{10}{1j\omega\left(1 + \frac{j\omega}{5}\right)}$$





Chapter 14, Solution 11.

$$\mathbf{H}(\omega) = \frac{5(1 + j\omega/10)}{j\omega(1 + j\omega/2)}$$

$$H_{dB} = 20 \log_{10} 5 + 20 \log_{10} |1 + j\omega/10| - 20 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/2|$$

$$\phi = -90^\circ + \tan^{-1} \omega/10 - \tan^{-1} \omega/2$$

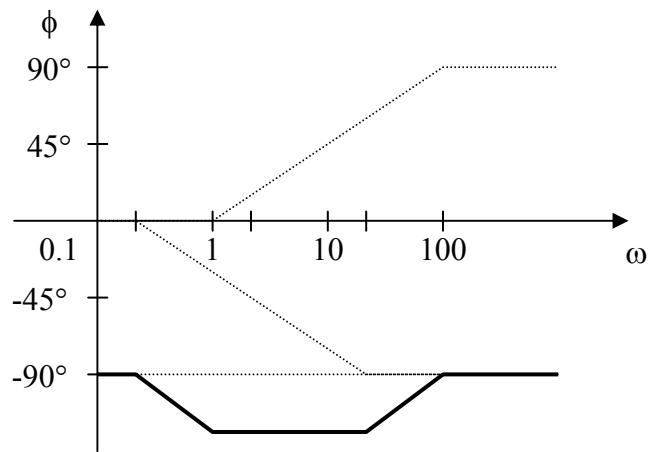
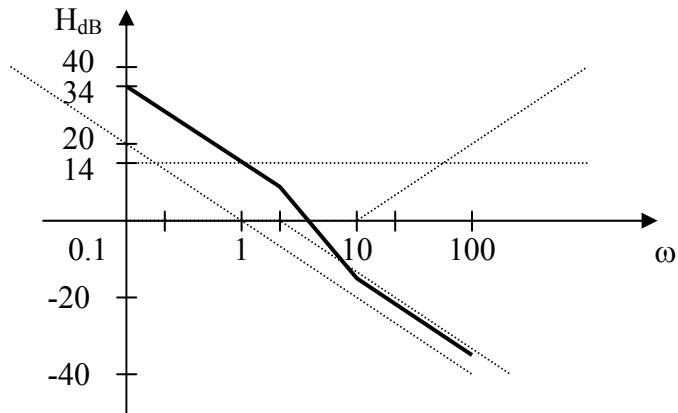
The magnitude and phase plots are shown below.



Chapter 14, Solution 12.

$$T(\omega) = \frac{0.1(1 + j\omega)}{j\omega(1 + j\omega/10)}, \quad 20 \log 0.1 = -20$$

The plots are shown below.

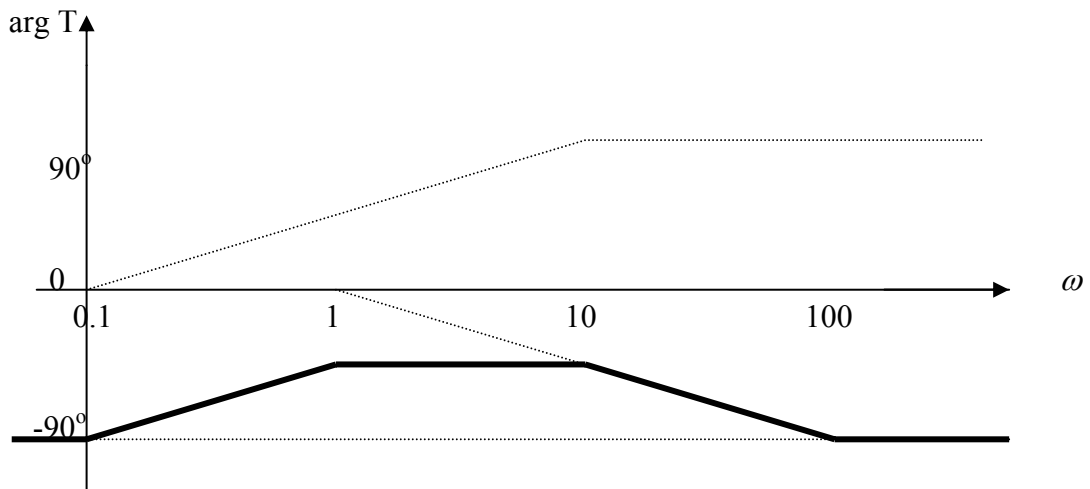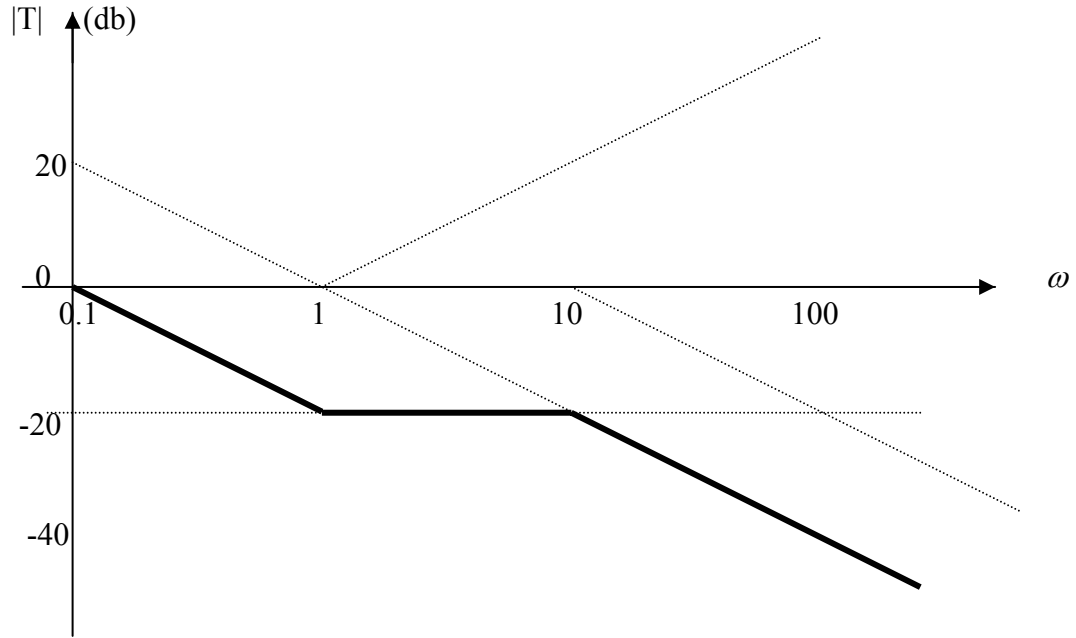


Chapter 14, Solution 13.

$$G(\omega) = \frac{1 + j\omega}{(j\omega)^2(10 + j\omega)} = \frac{(1/10)(1 + j\omega)}{(j\omega)^2(1 + j\omega/10)}$$

$$G_{dB} = -20 + 20 \log_{10} |1 + j\omega| - 40 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/10|$$
$$\phi = -180^\circ + \tan^{-1} \omega - \tan^{-1} \omega/10$$

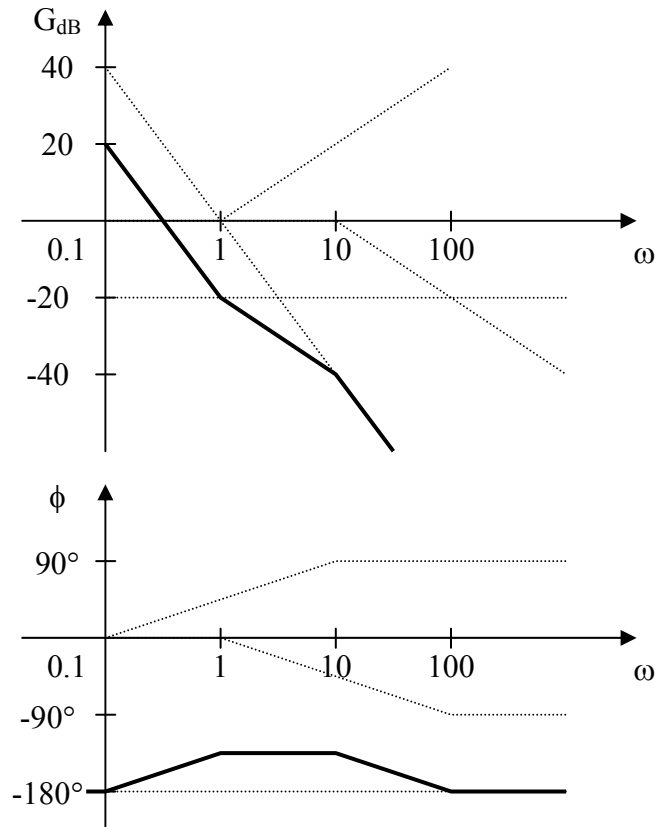The magnitude and phase plots are shown below.




Chapter 14, Solution 14.

$$\mathbf{H}(\omega) = \frac{50}{25} \frac{1 + j\omega}{j\omega \left(1 + \frac{j\omega 10}{25} + \left(\frac{j\omega}{5} \right)^2 \right)}$$

$$\begin{aligned} H_{dB} &= 20 \log_{10} 2 + 20 \log_{10} |1 + j\omega| - 20 \log_{10} |j\omega| \\ &\quad - 20 \log_{10} \left| 1 + j\omega 2/5 + (j\omega/5)^2 \right| \end{aligned}$$

$$\phi = -90^\circ + \tan^{-1} \omega - \tan^{-1} \left(\frac{\omega 10/25}{1 - \omega^2/5} \right)$$

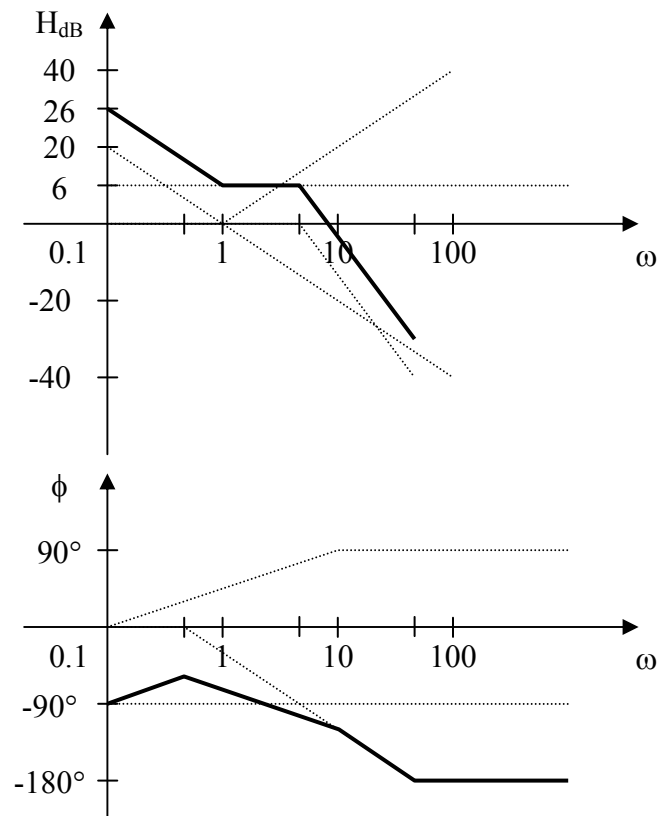The magnitude and phase plots are shown below.




Chapter 14, Solution 15.

$$\mathbf{H}(\omega) = \frac{40(1 + j\omega)}{(2 + j\omega)(10 + j\omega)} = \frac{2(1 + j\omega)}{(1 + j\omega/2)(1 + j\omega/10)}$$

$$H_{dB} = 20 \log_{10} 2 + 20 \log_{10} |1 + j\omega| - 20 \log_{10} |1 + j\omega/2| - 20 \log_{10} |1 + j\omega/10|$$


$$\phi = \tan^{-1} \omega - \tan^{-1} \omega/2 - \tan^{-1} \omega/10$$

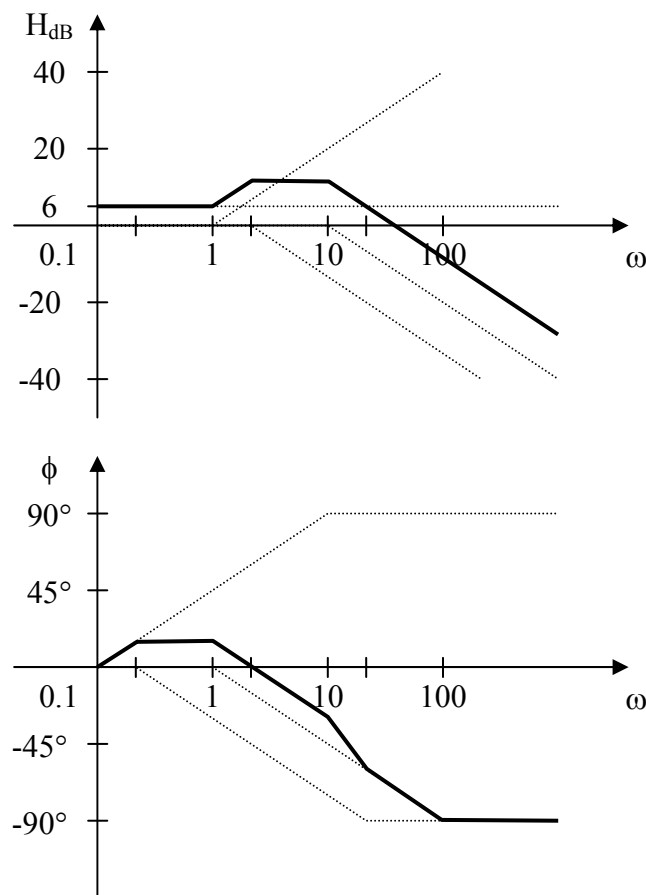The magnitude and phase plots are shown below.



Chapter 14, Solution 16.
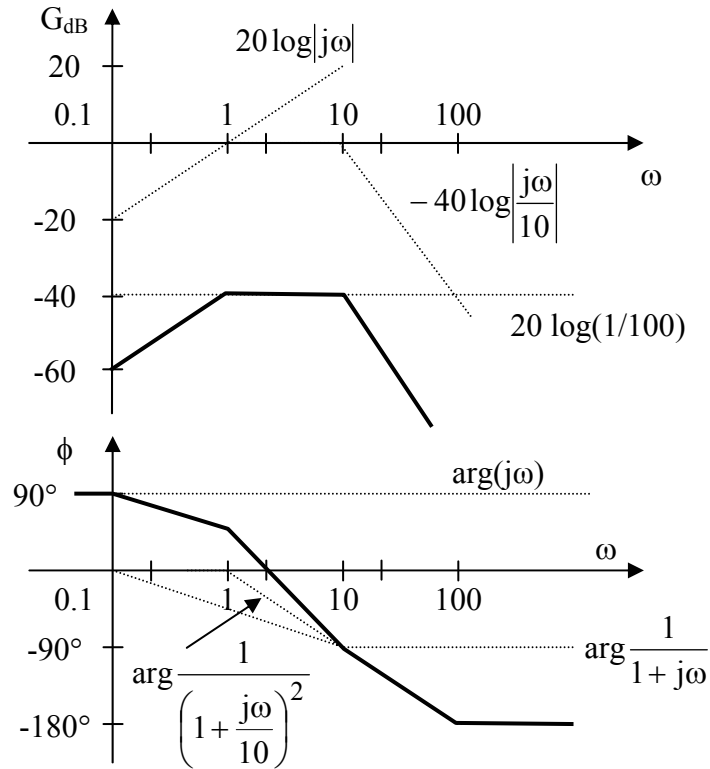
$$G(\omega) = \frac{j\omega}{100(1 + j\omega)\left(1 + \frac{j\omega}{10}\right)^2}$$




Chapter 14, Solution 17.


$$G(\omega) = \frac{(1/4)j\omega}{(1+j\omega)(1+j\omega/2)^2}$$

$$G_{dB} = -20 \log_{10} 4 + 20 \log_{10} |j\omega| - 20 \log_{10} |1+j\omega| - 40 \log_{10} |1+j\omega/2|$$

$$\phi = -90^\circ - \tan^{-1} \omega - 2 \tan^{-1} \omega/2$$

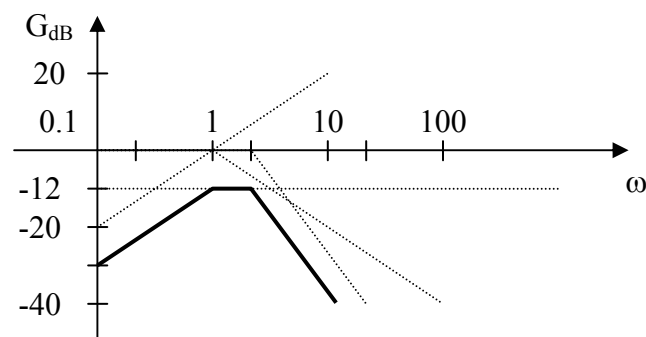The magnitude and phase plots are shown below.



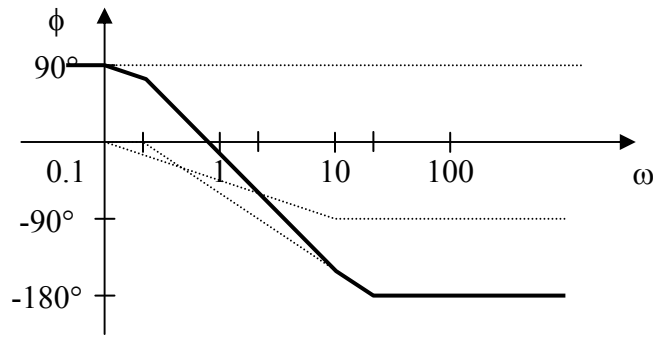

Chapter 14, Solution 18.


$$G(\omega) = \frac{4(1 + j\omega/2)^2}{50j\omega(1 + j\omega/5)(1 + j\omega/10)}$$

$$G_{dB} = 20 \log_{10} 4/50 + 40 \log_{10} |1 + j\omega/2| - 20 \log_{10} |j\omega| \\ - 20 \log_{10} |1 + j\omega/5| - 20 \log_{10} |1 + j\omega/10|$$

$$\text{where } 20 \log_{10} 4/50 = -21.94$$

$$\phi = -90^\circ + 2 \tan^{-1} \omega/2 - \tan^{-1} \omega/5 - \tan^{-1} \omega/10$$

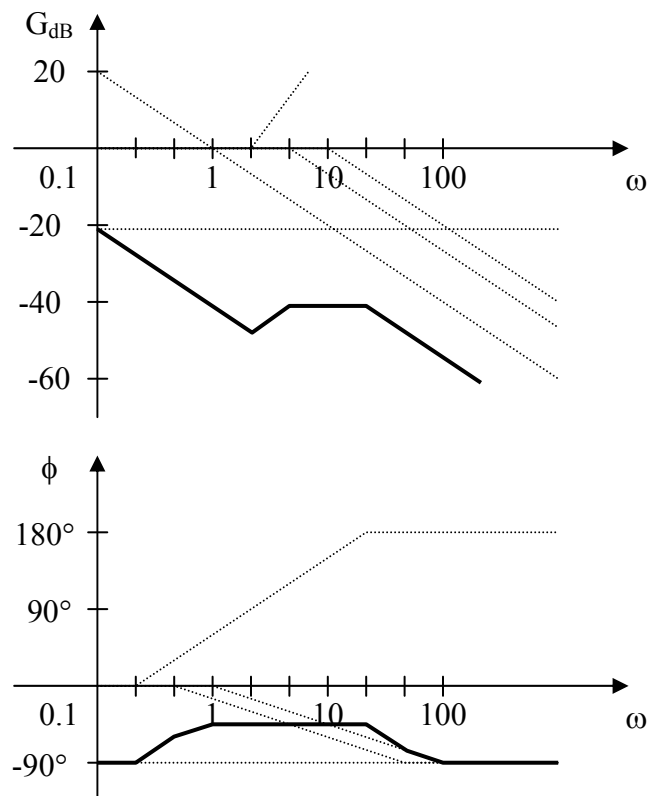The magnitude and phase plots are shown below.




Chapter 14, Solution 19.

$$\mathbf{H}(\omega) = \frac{j\omega}{100(1 + j\omega/10 - \omega^2/100)}$$

$$H_{\text{dB}} = 20 \log_{10} |j\omega| - 20 \log_{10} 100 - 20 \log_{10} |1 + j\omega/10 - \omega^2/100|$$

$$\phi = 90^\circ - \tan^{-1} \left(\frac{\omega/10}{1 - \omega^2/100} \right)$$

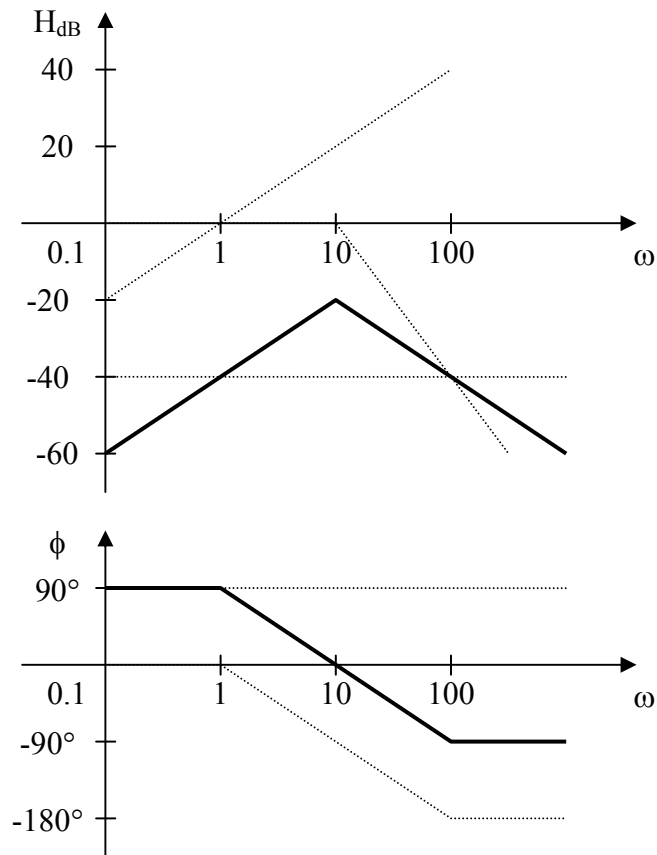The magnitude and phase plots are shown below.




Chapter 14, Solution 20.

$$N(\omega) = \frac{10(1 + j\omega - \omega^2)}{(1 + j\omega)(1 + j\omega/10)}$$

$$N_{dB} = 20 - 20 \log_{10} |1 + j\omega| - 20 \log_{10} |1 + j\omega/10| + 20 \log_{10} |1 + j\omega - \omega^2|$$

$$\phi = \tan^{-1} \left(\frac{\omega}{1 - \omega^2} \right) - \tan^{-1} \omega - \tan^{-1} \omega/10$$

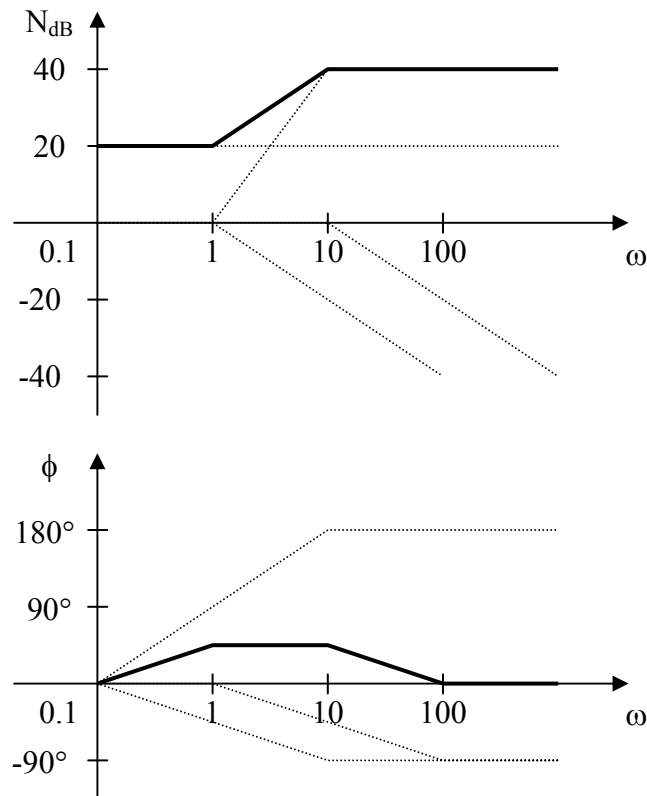The magnitude and phase plots are shown below.



Chapter 14, Solution 21.


$$T(\omega) = \frac{j\omega(1 + j\omega)}{100(1 + j\omega/10)(1 + j\omega/10 - \omega^2/100)}$$

$$T_{dB} = 20 \log_{10} |j\omega| + 20 \log_{10} |1 + j\omega| - 20 \log_{10} 100$$

$$-20 \log_{10} |1 + j\omega/10| - 20 \log_{10} |1 + j\omega/10 - \omega^2/100|$$

$$\phi = 90^\circ + \tan^{-1} \omega - \tan^{-1} \omega/10 - \tan^{-1} \left(\frac{\omega/10}{1 - \omega^2/100} \right)$$

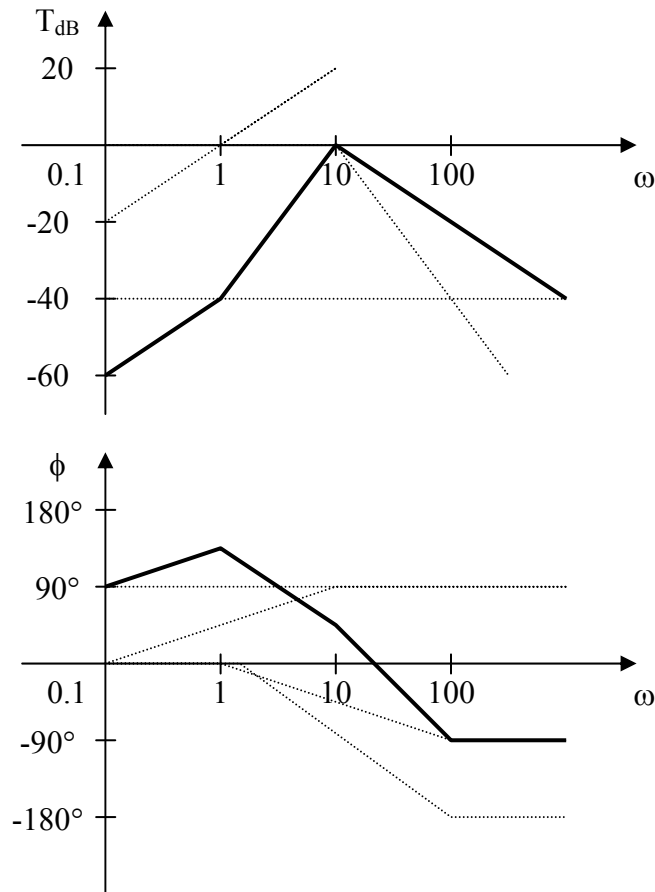The magnitude and phase plots are shown below.



Chapter 14, Solution 22.

$$20 = 20 \log_{10} k \longrightarrow k = 10$$

$$\text{A zero of slope } +20 \text{ dB/dec at } \omega = 2 \longrightarrow 1 + j\omega/2$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 20 \longrightarrow \frac{1}{1 + j\omega/20}$$

A pole of slope -20 dB/dec at $\omega = 100 \longrightarrow \frac{1}{1 + j\omega/100}$

Hence,

$$\mathbf{H}(\omega) = \frac{10(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{10^4 (2 + j\omega)}}{\mathbf{(20 + j\omega)(100 + j\omega)}}$$

Chapter 14, Solution 23.

A zero of slope +20 dB/dec at the origin $\longrightarrow j\omega$

A pole of slope -20 dB/dec at $\omega = 1 \longrightarrow \frac{1}{1 + j\omega/1}$

A pole of slope -40 dB/dec at $\omega = 10 \longrightarrow \frac{1}{(1 + j\omega/10)^2}$


Hence,

$$\mathbf{H}(\omega) = \frac{j\omega}{(1 + j\omega)(1 + j\omega/10)^2}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{100 j\omega}}{\mathbf{(1 + j\omega)(10 + j\omega)^2}}$$

Chapter 14, Solution 24.

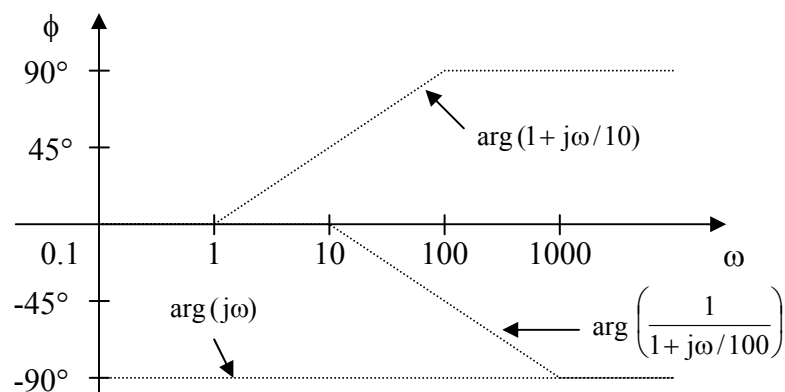The phase plot is decomposed as shown below.



$$G(\omega) = \frac{k'(1 + j\omega/10)}{j\omega(1 + j\omega/100)} = \frac{k'(10)(10 + j\omega)}{j\omega(100 + j\omega)}$$

where k' is a constant since $\arg k' = 0$.

Hence,
$$G(\omega) = \frac{\mathbf{k(10 + j\omega)}}{\mathbf{j\omega(100 + j\omega)}}$$
 where $\mathbf{k = 10k'}$ is constant

Chapter 14, Solution 25.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}} = 5 \text{ krad/s}$$

$$\mathbf{Z(\omega_0) = R = \underline{2 \text{ k}\Omega}}$$

$$\mathbf{Z(\omega_0/4) = R + j\left(\frac{\omega_0}{4}L - \frac{4}{\omega_0 C}\right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j\left(\frac{5 \times 10^3}{4} \cdot 40 \times 10^{-3} - \frac{4}{(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j(50 - 4000/5)}$$

$$\mathbf{Z(\omega_0/4) = \underline{2 - j0.75 \text{ k}\Omega}}$$

$$\mathbf{Z(\omega_0/2) = R + j\left(\frac{\omega_0}{2}L - \frac{2}{\omega_0 C}\right)}$$

$$\mathbf{Z(\omega_0/2) = 2000 + j\left(\frac{(5 \times 10^3)}{2}(40 \times 10^{-3}) - \frac{2}{(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(\omega_0/2) = 2000 + j(100 - 2000/5)}$$

$$\mathbf{Z(\omega_0/2) = \underline{2 - j0.3 \text{ k}\Omega}}$$

$$\mathbf{Z(2\omega_0) = R + j\left(2\omega_0 L - \frac{1}{2\omega_0 C}\right)}$$

$$\mathbf{Z}(2\omega_0) = 2000 + j \left((2)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(2)(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(2\omega_0) = \underline{\underline{2 + j0.3 \text{ k}\Omega}}$$

$$\mathbf{Z}(4\omega_0) = R + j \left(4\omega_0 L - \frac{1}{4\omega_0 C} \right)$$

$$\mathbf{Z}(4\omega_0) = 2000 + j \left((4)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(4)(5 \times 10^3)(1 \times 10^{-6})} \right)$$

$$\mathbf{Z}(4\omega_0) = \underline{\underline{2 + j0.75 \text{ k}\Omega}}$$

Chapter 14, Solution 26.

$$(a) \quad f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{5 \times 10^{-9} \times 10 \times 10^{-3}}} = \underline{\underline{22.51 \text{ kHz}}}$$

$$(b) \quad B = \frac{R}{L} = \frac{100}{10 \times 10^{-3}} = \underline{\underline{10 \text{ krad/s}}}$$

$$(c) \quad Q = \frac{\omega_o L}{R} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{10^6}{\sqrt{50}} \frac{10 \times 10^{-3}}{0.1 \times 10^3} = \underline{\underline{14.142}}$$

Chapter 14, Solution 27.

At resonance,

$$\mathbf{Z} = R = 10 \Omega, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = \frac{R}{L} \quad \text{and} \quad Q = \frac{\omega_0}{B} = \frac{\omega_0 L}{R}$$

Hence,

$$L = \frac{RQ}{\omega_0} = \frac{(10)(80)}{50} = 16 \text{ H}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(50)^2 (16)} = 25 \mu\text{F}$$

$$B = \frac{R}{L} = \frac{10}{16} = 0.625 \text{ rad/s}$$

Therefore,

$$R = \underline{10 \Omega}, \quad L = \underline{16 \text{ H}}, \quad C = \underline{25 \mu\text{F}}, \quad B = \underline{0.625 \text{ rad/s}}$$

Chapter 14, Solution 28.

Let $R = 10 \Omega$.

$$L = \frac{R}{B} = \frac{10}{20} = 0.5 \text{ H}$$


$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(1000)^2 (0.5)} = 2 \mu\text{F}$$

$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$

Therefore, if $R = 10 \Omega$ then

$$L = \underline{0.5 \text{ H}}, \quad C = \underline{2 \mu\text{F}}, \quad Q = \underline{50}$$

Chapter 14, Solution 29.

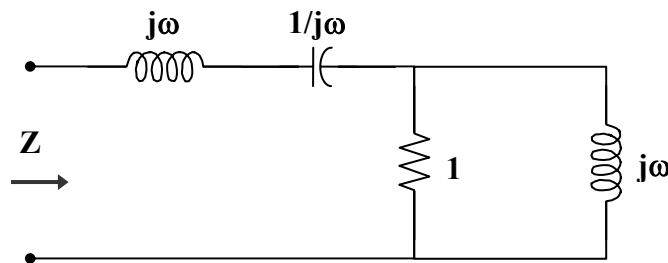

$$Z = j\omega + \frac{1}{j\omega} + \frac{j\omega}{1 + j\omega}$$

$$\mathbf{Z} = j\left(\omega - \frac{1}{\omega}\right) + \frac{\omega^2 + j\omega}{1 + \omega^2}$$

Since $v(t)$ and $i(t)$ are in phase,

$$\text{Im}(\mathbf{Z}) = 0 = \omega - \frac{1}{\omega} + \frac{\omega}{1 + \omega^2}$$

$$\omega^4 + \omega^2 - 1 = 0$$

$$\omega^2 = \frac{-1 \pm \sqrt{1+4}}{2} = 0.618$$

$$\omega = \underline{\underline{\mathbf{0.7861 \text{ rad/s}}}}$$

Chapter 14, Solution 30.

Select $R = 10 \Omega$.

$$L = \frac{R}{\omega_0 Q} = \frac{10}{(10)(20)} = 0.05 \text{ H} = 5 \text{ mH}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(100)(0.05)} = 0.2 \text{ F}$$

$$B = \frac{1}{RC} = \frac{1}{(10)(0.2)} = 0.5 \text{ rad/s}$$

Therefore, if $R = 10 \Omega$ then

$$L = \underline{\underline{\mathbf{5 \text{ mH}}}}, \quad C = \underline{\underline{\mathbf{0.2 \text{ F}}}}, \quad B = \underline{\underline{\mathbf{0.5 \text{ rad/s}}}}$$

Chapter 14, Solution 31.

$$X_L = \omega L \quad \longrightarrow \quad L = \frac{X_L}{\omega}$$

$$B = \frac{R}{L} = \frac{\omega R}{X_L} = \frac{2\pi \times 10 \times 10^6 \times 5.6 \times 10^3}{40 \times 10^3} = \underline{\underline{\mathbf{8.796 \times 10^6 \text{ rad/s}}}}$$

Chapter 14, Solution 32.

Since $Q > 10$,

$$\omega_1 = \omega_0 - \frac{B}{2}, \quad \omega_2 = \omega_0 + \frac{B}{2}$$

$$B = \frac{\omega_0}{Q} = \frac{6 \times 10^6}{120} = \underline{\underline{50 \text{ krad/s}}}$$

$$\omega_1 = 6 - 0.025 = \underline{\underline{5.975 \times 10^6 \text{ rad/s}}}$$

$$\omega_2 = 6 + 0.025 = \underline{\underline{6.025 \times 10^6 \text{ rad/s}}}$$

Chapter 14, Solution 33.

$$Q = \omega_0 RC \longrightarrow C = \frac{Q}{2\pi f_0 R} = \frac{80}{2\pi \times 5.6 \times 10^6 \times 40 \times 10^3} = \underline{\underline{56.84 \text{ pF}}}$$

$$Q = \frac{R}{\omega_0 L} \longrightarrow L = \frac{R}{2\pi f_0 Q} = \frac{40 \times 10^3}{2\pi \times 5.6 \times 10^6 \times 80} = \underline{\underline{14.21 \text{ }\mu\text{H}}}$$

Chapter 14, Solution 34.

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 10^{-3} \times 60 \times 10^{-6}}} = \underline{\underline{1.443 \text{ krad/s}}}$$

$$(b) \quad B = \frac{1}{RC} = \frac{1}{5 \times 10^3 \times 60 \times 10^{-6}} = \underline{\underline{3.33 \text{ rad/s}}}$$

$$(c) \quad Q = \omega_0 RC = 1.443 \times 10^3 \times 5 \times 10^3 \times 60 \times 10^{-6} = \underline{\underline{432.9}}$$

Chapter 14, Solution 35.

At resonance,

$$Y = \frac{1}{R} \longrightarrow R = \frac{1}{Y} = \frac{1}{25 \times 10^{-3}} = \underline{\underline{40 \Omega}}$$

$$Q = \omega_0 RC \longrightarrow C = \frac{Q}{\omega_0 R} = \frac{80}{(200 \times 10^3)(40)} = \underline{\underline{10 \mu F}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C} = \frac{1}{(4 \times 10^{10})(10 \times 10^{-6})} = \underline{\underline{2.5 \mu H}}$$

$$B = \frac{\omega_0}{Q} = \frac{200 \times 10^3}{80} = \underline{\underline{2.5 \text{ krad/s}}}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 200 - 2.5 = \underline{\underline{197.5 \text{ krad/s}}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 200 + 2.5 = \underline{\underline{202.5 \text{ krad/s}}}$$

Chapter 14, Solution 36.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 5000 \text{ rad/s}$$

$$Y(\omega_0) = \frac{1}{R} \longrightarrow Z(\omega_0) = R = \underline{\underline{2 \text{ k}\Omega}}$$

$$Y(\omega_0/4) = \frac{1}{R} + j \left(\frac{\omega_0}{4} C - \frac{4}{\omega_0 L} \right) = 0.5 - j18.75 \text{ kS}$$

$$Z(\omega_0/4) = \frac{1}{0.0005 - j0.01875} = \underline{\underline{1.4212 + j53.3 \Omega}}$$

$$Y(\omega_0/2) = \frac{1}{R} + j \left(\frac{\omega_0}{2} C - \frac{2}{\omega_0 L} \right) = 0.5 - j7.5 \text{ kS}$$

$$\mathbf{Z}(\omega_0/2) = \frac{1}{0.0005 - j0.0075} = \underline{\underline{\mathbf{8.85 + j132.74 \Omega}}}$$

$$\mathbf{Y}(2\omega_0) = \frac{1}{R} + j\left(2\omega_0L - \frac{1}{2\omega_0C}\right) = 0.5 + j7.5 \text{ kS}$$

$$\mathbf{Z}(2\omega_0) = \underline{\underline{\mathbf{8.85 - j132.74 \Omega}}}$$

$$\mathbf{Y}(4\omega_0) = \frac{1}{R} + j\left(4\omega_0L - \frac{1}{4\omega_0C}\right) = 0.5 + j18.75 \text{ kS}$$

$$\mathbf{Z}(4\omega_0) = \underline{\underline{\mathbf{1.4212 - j53.3 \Omega}}}$$

Chapter 14, Solution 37.

$$Z = j\omega L // \left(R + \frac{1}{j\omega C}\right) = \frac{j\omega L \left(R + \frac{1}{j\omega C}\right)}{R + \frac{1}{j\omega C} + j\omega L} = \frac{\left(\frac{L}{C} + j\omega LR\right) \left(R + j\left(\omega L - \frac{1}{\omega C}\right)\right)}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{Im}(Z) = \frac{\omega LR^2 + \frac{L}{C} \left(\omega L - \frac{1}{\omega C}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = 0 \quad \longrightarrow \quad \omega^2(R^2C^2 + LC) = 1$$

Thus,

$$\omega = \frac{1}{\sqrt{LC + R^2C^2}}$$

Chapter 14, Solution 38.

$$\mathbf{Y} \frac{1}{R + j\omega L} + j\omega C = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2L^2}$$

At resonance, $\text{Im}(\mathbf{Y}) = 0$, i.e.

$$\omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \sqrt{\frac{1}{(40 \times 10^{-3})(10 \times 10^{-6})} - \left(\frac{50}{40 \times 10^{-3}}\right)^2}$$

$$\omega_0 = \underline{\underline{4841 \text{ rad/s}}}$$

Chapter 14, Solution 39.

$$(a) \quad B = \omega_2 - \omega_1 = 2\pi(f_2 - f_1) = 2\pi(90 - 86) \times 10^3 = 8\pi \text{krad/s}$$

$$\omega_0 = \frac{1}{2}(\omega_1 + \omega_2) = 2\pi(88) \times 10^3 = 176\pi$$

$$B = \frac{1}{RC} \quad \longrightarrow \quad C = \frac{1}{BR} = \frac{1}{8\pi \times 10^3 \times 2 \times 10^3} = \underline{\underline{19.89 \text{nF}}}$$

$$(b) \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \longrightarrow \quad L = \frac{1}{\omega_0^2 C} = \frac{1}{(176\pi)^2 \times 19.89 \times 10^{-9}} = \underline{\underline{164.4 \text{H}}}$$

$$(c) \quad \omega_0 = 176\pi = \underline{\underline{552.9 \text{krad/s}}}$$

$$(d) \quad B = 8\pi = \underline{\underline{25.13 \text{krad/s}}}$$

$$(e) \quad Q = \frac{\omega_0}{B} = \frac{176\pi}{8\pi} = \underline{\underline{22}}$$

Chapter 14, Solution 40.

$$(a) \quad L = 5 + 10 = 15 \text{ mH}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{15 \times 10^{-3} \times 20 \times 10^{-6}}} = \underline{\underline{1.8257 \text{ k rad/sec}}}$$

$$Q = \omega_0 RC = 1.8257 \times 10^3 \times 25 \times 10^3 \times 20 \times 10^{-6} = \underline{\underline{912.8}}$$

$$B = \frac{1}{RC} = \frac{1}{25 \times 10^3 \times 20 \times 10^{-6}} = \underline{\underline{2 \text{ rad}}}$$

- (b) To increase B by 100% means that $B' = 4$.

$$C' = \frac{1}{RB'} = \frac{1}{25 \times 10^3 \times 4} = \underline{\underline{10 \mu\text{F}}}$$

Since $C' = \frac{C_1 C_2}{C_1 + C_2} = 10 \mu\text{F}$ and $C_1 = 20 \mu\text{F}$, we then obtain $C_2 = 20 \mu\text{F}$.

Therefore, to increase the bandwidth, we merely **add another 20 μF in series with the first one.**

Chapter 14, Solution 41.

- (a) This is a series RLC circuit.

$$R = 2 + 6 = 8 \Omega, \quad L = 1 \text{ H}, \quad C = 0.4 \text{ F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4}} = \underline{\underline{1.5811 \text{ rad/s}}}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1.5811}{8} = \underline{\underline{0.1976}}$$

$$B = \frac{R}{L} = \underline{\underline{8 \text{ rad/s}}}$$

- (b) This is a parallel RLC circuit.

$$3 \mu\text{F} \text{ and } 6 \mu\text{F} \longrightarrow \frac{(3)(6)}{3+6} = 2 \mu\text{F}$$

$$C = 2 \mu\text{F}, \quad R = 2 \text{ k}\Omega, \quad L = 20 \text{ mH}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-6})(20 \times 10^{-3})}} = \underline{\underline{5 \text{ krad/s}}}$$

$$Q = \frac{R}{\omega_0 L} = \frac{2 \times 10^3}{(5 \times 10^3)(20 \times 10^{-3})} = \underline{\underline{20}}$$

$$B = \frac{1}{RC} = \frac{1}{(2 \times 10^3)(2 \times 10^{-6})} = \underline{\underline{250 \text{ krad/s}}}$$

Chapter 14, Solution 42.

(a) $\mathbf{Z}_{in} = (1/j\omega C) \parallel (R + j\omega L)$

$$\mathbf{Z}_{in} = \frac{\frac{R + j\omega L}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

$$\mathbf{Z}_{in} = \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

At resonance, $\text{Im}(\mathbf{Z}_{in}) = 0$, i.e.

$$0 = \omega L(1 - \omega^2 LC) - \omega R^2 C$$

$$\omega^2 LC = L - R^2 C$$

$$\omega_0 = \sqrt{\frac{L - R^2 C}{LC}} = \underline{\underline{\sqrt{\frac{1}{C} - \frac{R^2}{L}}}}$$

(b) $\mathbf{Z}_{in} = j\omega L \parallel (R + 1/j\omega C)$

$$\mathbf{Z}_{in} = \frac{j\omega L (R + 1/j\omega C)}{R + j\omega L + 1/j\omega C} = \frac{j\omega L (1 + j\omega RC)}{(1 - \omega^2 LC) + j\omega RC}$$

$$\mathbf{Z}_{in} = \frac{(-\omega^2 RLC + j\omega L)[(1 - \omega^2 LC) - j\omega RC]}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

At resonance, $\text{Im}(\mathbf{Z}_{in}) = 0$, i.e.

$$0 = \omega L(1 - \omega^2 LC) + \omega^3 R^2 C^2 L$$

$$\omega^2 (LC - R^2 C^2) = 1$$

$$\omega_0 = \frac{1}{\sqrt{LC - R^2 C^2}}$$

(c) $Z_{in} = R \parallel (j\omega L + 1/j\omega C)$

$$Z_{in} = \frac{R(j\omega L + 1/j\omega C)}{R + j\omega L + 1/j\omega C} = \frac{R(1 - \omega^2 LC)}{(1 - \omega^2 LC) + j\omega RC}$$

$$Z_{in} = \frac{R(1 - \omega^2 LC)[(1 - \omega^2 LC) - j\omega RC]}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

At resonance, $\text{Im}(Z_{in}) = 0$, i.e.


$$0 = R(1 - \omega^2 LC)\omega RC$$

$$1 - \omega^2 LC = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Chapter 14, Solution 43.

Consider the circuit below.

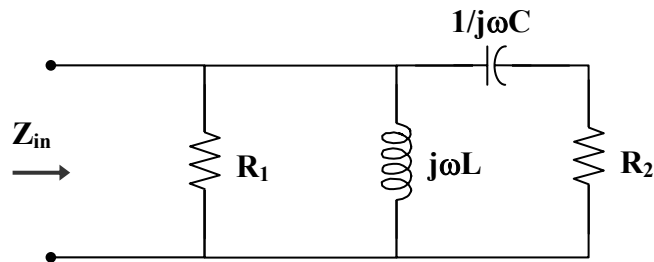

(a) $Z_{in} = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$

$$Z_{in} = \left(\frac{R_1 j\omega L}{R_1 + j\omega L} \right) \parallel \left(R_2 + \frac{1}{j\omega C} \right)$$

$$\mathbf{Z}_{in} = \frac{\frac{j\omega R_1 L}{R_1 + j\omega L} \cdot \left(R_2 + \frac{1}{j\omega C} \right)}{R_2 + \frac{1}{j\omega C} + \frac{jR_1 \omega L}{R_1 + j\omega L}}$$

$$\mathbf{Z}_{in} = \frac{j\omega R_1 L (1 + j\omega R_2 C)}{(R_1 + j\omega L)(1 + j\omega R_2 C) - \omega^2 L C R_1}$$

$$\mathbf{Z}_{in} = \frac{-\omega^2 R_1 R_2 L C + j\omega R_1 L}{R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 + j\omega (L + R_1 R_2 C)}$$

$$\mathbf{Z}_{in} = \frac{(-\omega^2 R_1 R_2 L C + j\omega R_1 L)[R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 - j\omega (L + R_1 R_2 C)]}{(R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)^2 + \omega^2 (L + R_1 R_2 C)^2}$$

At resonance, $\text{Im}(\mathbf{Z}_{in}) = 0$, i.e.

$$0 = \omega^3 R_1 R_2 L C (L + R_1 R_2 C) + \omega R_1 L (R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)$$

$$0 = \omega^3 R_1^2 R_2^2 L C^2 + R_1^2 \omega L - \omega^3 R_1^2 L^2 C$$

$$0 = \omega^2 R_2^2 C^2 + 1 - \omega^2 L C$$

$$\omega^2 (L C - R_2^2 C^2) = 1$$

$$\omega_0 = \frac{1}{\sqrt{L C - R_2^2 C^2}}$$

$$\omega_0 = \frac{1}{\sqrt{(0.02)(9 \times 10^{-6}) - (0.1)^2 (9 \times 10^{-6})^2}}$$

$$\omega_0 = \underline{\underline{2.357 \text{ krad/s}}}$$

(b) At $\omega = \omega_0 = 2.357 \text{ krad/s}$,

$$j\omega L = j(2.357 \times 10^3)(20 \times 10^{-3}) = j47.14$$

$$R_1 \parallel j\omega L = \frac{j47.14}{1 + j47.14} = 0.9996 + j0.0212$$

$$R_2 + \frac{1}{j\omega C} = 0.1 + \frac{1}{j(2.357 \times 10^3)(9 \times 10^{-6})} = 0.1 - j47.14$$


$$\mathbf{Z}_{in}(\omega_0) = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$$

$$\mathbf{Z}_{in}(\omega_0) = \frac{(0.9996 + j0.0212)(0.1 - j47.14)}{(0.9996 + j0.0212) + (0.1 - j47.14)}$$

$$\mathbf{Z}_{in}(\omega_0) = \underline{\underline{\mathbf{1} \Omega}}$$

Chapter 14, Solution 44.

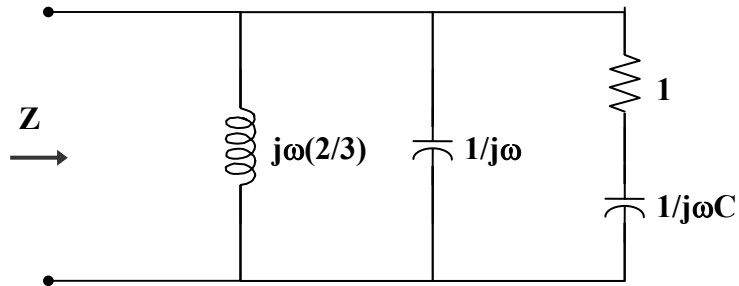We find the input impedance of the circuit shown below.



$$\frac{1}{\mathbf{Z}} = \frac{3}{j\omega 2} + j\omega + \frac{1}{1 + 1/j\omega C}, \quad \omega = 1$$

$$\frac{1}{\mathbf{Z}} = -j1.5 + j + \frac{jC}{1 + jC} = -j0.5 + \frac{C^2 + jC}{1 + C^2}$$

$v(t)$ and $i(t)$ are in phase when \mathbf{Z} is purely real, i.e.

$$0 = -0.5 + \frac{C}{1 + C^2} \longrightarrow (C - 1)^2 = 1 \quad \text{or} \quad C = \underline{\underline{\mathbf{1} \text{ F}}}$$

$$\frac{1}{\mathbf{Z}} = \frac{C^2}{1 + C^2} = \frac{1}{2} \longrightarrow \mathbf{Z} = 2 \Omega$$


$$\mathbf{V} = \mathbf{Z}\mathbf{I} = (2)(10) = 20$$

$$v(t) = 20 \sin(t) \text{ V}, \quad \text{i.e.} \quad V_o = \underline{\underline{\mathbf{20} \text{ V}}}$$

Chapter 14, Solution 45.

$$(a) \quad 1 \parallel j\omega = \frac{j\omega}{1+j\omega}, \quad 1 \parallel \frac{1}{j\omega} = \frac{1/j\omega}{1+1/j\omega} = \frac{1}{1+j\omega}$$

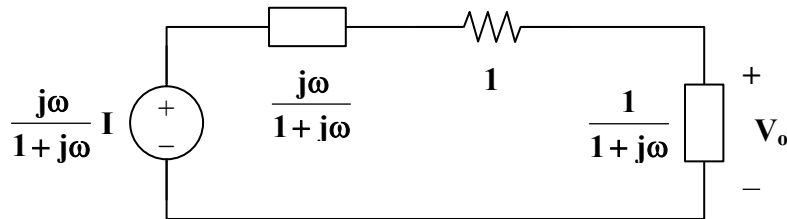Transform the current source gives the circuit below.



$$V_o = \frac{\frac{1}{1+j\omega}}{1 + \frac{1}{1+j\omega} + \frac{j\omega}{1+j\omega}} \cdot \frac{j\omega}{1+j\omega} I$$

$$H(\omega) = \frac{V_o}{I} = \frac{j\omega}{2(1+j\omega)^2}$$

$$(b) \quad H(1) = \frac{1}{2(1+j)^2}$$

$$|H(1)| = \frac{1}{2(\sqrt{2})^2} = \underline{\underline{0.25}}$$

Chapter 14, Solution 46.

(a) This is an RLC series circuit.

$$\omega_o = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega_o^2 L} = \frac{1}{(2\pi \times 15 \times 10^3)^2 \times 10 \times 10^{-3}} = \underline{\underline{11.26 \text{ nF}}}$$

$$(b) \quad Z = R, \quad I = V/Z = 120/20 = \underline{\underline{6 \text{ A}}}$$

$$(c) \quad Q = \frac{\omega_o L}{R} = \frac{2\pi \times 15 \times 10^3 \times 10 \times 10^{-3}}{20} = 15\pi = \underline{\underline{47.12}}$$

Chapter 14, Solution 47.

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{\mathbf{R}}{\mathbf{R} + j\omega\mathbf{L}} = \frac{1}{1 + j\omega\mathbf{L}/\mathbf{R}}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

At the corner frequency, $|H(\omega_c)| = \frac{1}{\sqrt{2}}$, i.e.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c\mathbf{L}}{\mathbf{R}}\right)^2}} \longrightarrow 1 = \frac{\omega_c\mathbf{L}}{\mathbf{R}} \quad \text{or} \quad \omega_c = \frac{\mathbf{R}}{\mathbf{L}}$$

Hence,

$$\omega_c = \frac{\mathbf{R}}{\mathbf{L}} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{\mathbf{R}}{\mathbf{L}} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3}{2 \times 10^{-3}} = \underline{\underline{796 \text{ kHz}}}$$

Chapter 14, Solution 48.

$$\mathbf{H}(\omega) = \frac{\mathbf{R} \parallel \frac{1}{j\omega\mathbf{C}}}{j\omega\mathbf{L} + \mathbf{R} \parallel \frac{1}{j\omega\mathbf{C}}}$$

$$\mathbf{H}(\omega) = \frac{\frac{\mathbf{R}/j\omega\mathbf{C}}{\mathbf{R} + 1/j\omega\mathbf{C}}}{j\omega\mathbf{L} + \frac{\mathbf{R}/j\omega\mathbf{C}}{\mathbf{R} + 1/j\omega\mathbf{C}}}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{R}}{\underline{\underline{\mathbf{R} + j\omega\mathbf{L} - \omega^2\mathbf{RLC}}}}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

Chapter 14, Solution 49.

$$\text{At dc, } H(0) = \frac{4}{2} = 2.$$

$$\text{Hence, } |H(\omega)| = \frac{1}{\sqrt{2}} H(0) = \frac{2}{\sqrt{2}}$$

$$\frac{2}{\sqrt{2}} = \frac{4}{\sqrt{4+100\omega_c^2}}$$

$$4 + 100\omega_c^2 = 8 \longrightarrow \omega_c = 0.2$$

$$H(2) = \frac{4}{2 + j20} = \frac{2}{1 + j10}$$

$$|H(2)| = \frac{2}{\sqrt{101}} = 0.199$$

$$\text{In dB, } 20 \log_{10} |H(2)| = \underline{\underline{-14.023}}$$

$$\arg H(2) = -\tan^{-1} 10 = \underline{\underline{-84.3^\circ}}$$

Chapter 14, Solution 50.

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L}$$

$H(0) = 0$ and $H(\infty) = 1$ showing that **this circuit is a highpass filter.**

$$H(\omega_c) = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

$$\text{or } \omega_c = \frac{R}{L} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{200}{0.1} = \underline{\underline{318.3 \text{ Hz}}}$$

Chapter 14, Solution 51.

$$\mathbf{H}'(\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega}{j\omega + 1/RC} \quad (\text{from Eq. 14.52})$$

This has a unity passband gain, i.e. $H(\infty) = 1$.

$$\frac{1}{RC} = \omega_c = 50$$

$$\mathbf{H}^{\wedge}(\omega) = 10 \mathbf{H}'(\omega) = \frac{j10\omega}{50 + j\omega}$$

$$\mathbf{H}(\omega) = \frac{j10\omega}{\underline{50 + j\omega}}$$

Chapter 14, Problem 52.

Design an RL lowpass filter that uses a 40-mH coil and has a cut-off frequency of 5 kHz.

Chapter 14, Solution 53.

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$R = 2\pi f_c L = (2\pi)(10^5)(40 \times 10^{-3}) = \underline{\underline{25.13 \text{ k}\Omega}}$$

Chapter 14, Solution 54.

$$\omega_1 = 2\pi f_1 = 20\pi \times 10^3$$

$$\omega_2 = 2\pi f_2 = 22\pi \times 10^3$$

$$B = \omega_2 - \omega_1 = 2\pi \times 10^3$$

$$\omega_0 = \frac{\omega_2 + \omega_1}{2} = 21\pi \times 10^3$$

$$Q = \frac{\omega_0}{B} = \frac{21\pi}{2\pi} = \underline{11.5}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C}$$

$$L = \frac{1}{(21\pi \times 10^3)^2 (80 \times 10^{-12})} = \underline{2.872 \text{ H}}$$

$$B = \frac{R}{L} \longrightarrow R = BL$$

$$R = (2\pi \times 10^3)(2.872) = \underline{18.045 \text{ k}\Omega}$$

Chapter 14, Solution 55.

$$\omega_c = 2\pi f_c = \frac{1}{RC} \longrightarrow R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi \times 2 \times 10^3 \times 300 \times 10^{-12}} = \underline{265.3 \text{ k}\Omega}$$

Chapter 14, Solution 56.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(25 \times 10^{-3})(0.4 \times 10^{-6})}} = 10 \text{ krad/s}$$

$$B = \frac{R}{L} = \frac{10}{25 \times 10^{-3}} = 0.4 \text{ krad/s}$$

$$Q = \frac{10}{0.4} = \underline{25}$$

$$\omega_1 = \omega_0 - B/2 = 10 - 0.2 = 9.8 \text{ krad/s} \quad \text{or} \quad f_1 = \frac{9.8}{2\pi} = 1.56 \text{ kHz}$$

$$\omega_2 = \omega_0 + B/2 = 10 + 0.2 = 10.2 \text{ krad/s} \quad \text{or} \quad f_2 = \frac{10.2}{2\pi} = 1.62 \text{ kHz}$$

Therefore,

$$\underline{1.56 \text{ kHz} < f < 1.62 \text{ kHz}}$$

Chapter 14, Solution 57.

(a) From Eq 14.54,

$$\mathbf{H}(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{sRC}{1 + sRC + s^2LC} = \frac{s\frac{R}{L}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

Since $B = \frac{R}{L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$,

$$\mathbf{H}(s) = \frac{s\mathbf{B}}{s^2 + s\mathbf{B} + \omega_0^2}$$


(b) From Eq. 14.56,

$$\mathbf{H}(s) = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{s^2 + \frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$\mathbf{H}(s) = \frac{s^2 + \omega_0^2}{s^2 + s\mathbf{B} + \omega_0^2}$$

Chapter 14, Solution 58.

(a) Consider the circuit below.

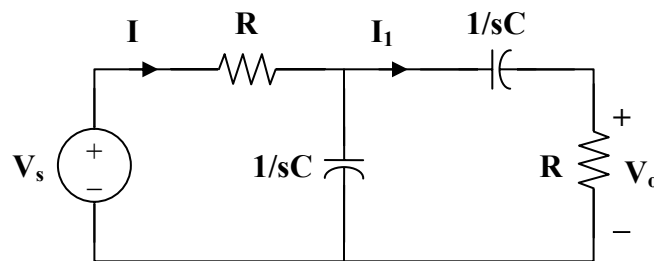

$$\mathbf{Z}(s) = R + \frac{1}{sC} \parallel \left(R + \frac{1}{sC} \right) = R + \frac{\frac{1}{sC} \left(R + \frac{1}{sC} \right)}{R + \frac{2}{sC}}$$

$$\mathbf{Z}(s) = R + \frac{1 + sRC}{sC(2 + sRC)}$$

$$\mathbf{Z}(s) = \frac{1 + 3sRC + s^2R^2C^2}{sC(2 + sRC)}$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}}$$

$$\mathbf{I}_1 = \frac{1/sC}{2/sC + R} \mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}(2 + sRC)}$$

$$\mathbf{V}_o = \mathbf{I}_1 R = \frac{R \mathbf{V}_s}{2 + sRC} \cdot \frac{sC(2 + sRC)}{1 + 3sRC + s^2R^2C^2}$$

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{sRC}{1 + 3sRC + s^2R^2C^2}$$

$$\mathbf{H}(s) = \frac{1}{3} \left[\frac{\frac{3}{RC} s}{s^2 + \frac{3}{RC} s + \frac{1}{R^2C^2}} \right]$$

$$\text{Thus, } \omega_0^2 = \frac{1}{R^2C^2} \quad \text{or} \quad \omega_0 = \frac{1}{RC} = \underline{\underline{1 \text{ rad/s}}}$$

$$B = \frac{3}{RC} = \underline{\underline{3 \text{ rad/s}}}$$

(b) Similarly,

$$\mathbf{Z}(s) = sL + R \parallel (R + sL) = sL + \frac{R(R + sL)}{2R + sL}$$

$$\mathbf{Z}(s) = \frac{R^2 + 3sRL + s^2L^2}{2R + sL}$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}}, \quad \mathbf{I}_1 = \frac{R}{2R + sL} \mathbf{I} = \frac{R \mathbf{V}_s}{\mathbf{Z}(2R + sL)}$$

$$\mathbf{V}_o = \mathbf{I}_1 \cdot sL = \frac{sLR \mathbf{V}_s}{2R + sL} \cdot \frac{2R + sL}{R^2 + 3sRL + s^2L^2}$$

$$\mathbf{H(s)} = \frac{\mathbf{V_o}}{\mathbf{V_s}} = \frac{\mathbf{sRL}}{\mathbf{R^2 + 3sRL + s^2L^2}} = \frac{\frac{1}{3}\left(\frac{3R}{L}s\right)}{\mathbf{s^2 + \frac{3R}{L}s + \frac{R^2}{L^2}}}$$

$$\text{Thus, } \omega_0 = \frac{R}{L} = \underline{\underline{\mathbf{1 \text{ rad/s}}}}$$

$$\mathbf{B} = \frac{3R}{L} = \underline{\underline{\mathbf{3 \text{ rad/s}}}}$$

Chapter 14, Solution 59.

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.1)(40 \times 10^{-12})}} = \underline{\underline{\mathbf{0.5 \times 10^6 \text{ rad/s}}}}$$

$$(b) \quad \mathbf{B} = \frac{R}{L} = \frac{2 \times 10^3}{0.1} = 2 \times 10^4$$

$$\mathbf{Q} = \frac{\omega_0}{\mathbf{B}} = \frac{0.5 \times 10^6}{2 \times 10^4} = 250$$

As a high Q circuit,

$$\omega_1 = \omega_0 - \frac{\mathbf{B}}{2} = 10^4 (50 - 1) = \underline{\underline{\mathbf{490 \text{ krad/s}}}}$$

$$\omega_2 = \omega_0 + \frac{\mathbf{B}}{2} = 10^4 (50 + 1) = \underline{\underline{\mathbf{510 \text{ krad/s}}}}$$

$$(c) \quad \text{As seen in part (b), } \mathbf{Q} = \underline{\underline{\mathbf{250}}}$$